

Special Diodes

**Semiconductor Devices and Circuits
(ECE 181302)**


10th December 2021

Special Purpose Diodes

- Besides rectification, a semiconductor diode has many other useful applications.
- Semiconductor diodes can be manufactured to regulate voltage or emit different colors of light.
- Examples of two special purpose diodes are
 - Light-emitting diode
 - Zener diode

Light Emitting Diode (LED)

- LED emits a certain color of light when forward-biased.
- Material is more exotic than silicon used in ordinary diodes/ transistors:
 - gallium arsenide (GaAs), gallium phosphide (GaP), or gallium arsenide phosphide (GaAsP)
 - typically 2-volt drop instead of 0.6 V drop
- Different semiconductor materials and different impurities result in different colours of light.
- When electron flows through LED, it loses energy by emitting a photon of light rather than by vibration of the crystal lattice (heat).
- LED efficiency is 30% (compare to incandescent bulb at 10%).

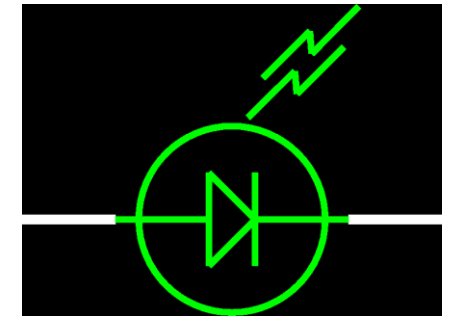

Zener Diode


- Zener diode is a special type of diode that is designed to work in reverse condition.
- Acts as a normal diode in the forward bias region.
- Designed to operate at voltages greater than the breakdown voltage (peak inverse voltage).
- It is heavily doped to have a thin depletion region, as a result breakdown voltage occurs at a lower voltage:
 - Operates at voltages that exceed breakdown voltage
 - Manufactured with a specific breakdown voltage (E_z)
 - Packaged like PN junction diodes
- The breakdown voltage is determined by the resistivity of the diode.
- Zener diodes are used to stabilize or regulate voltage.

Zener Diode Characteristics

- Schematic symbol:





(a)

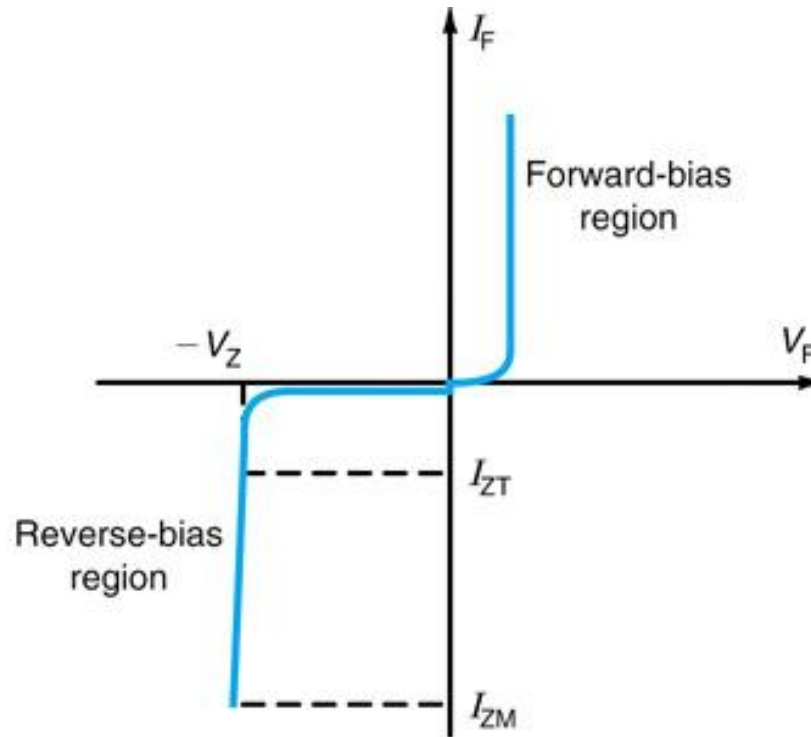

(b)


Voltage Regulation

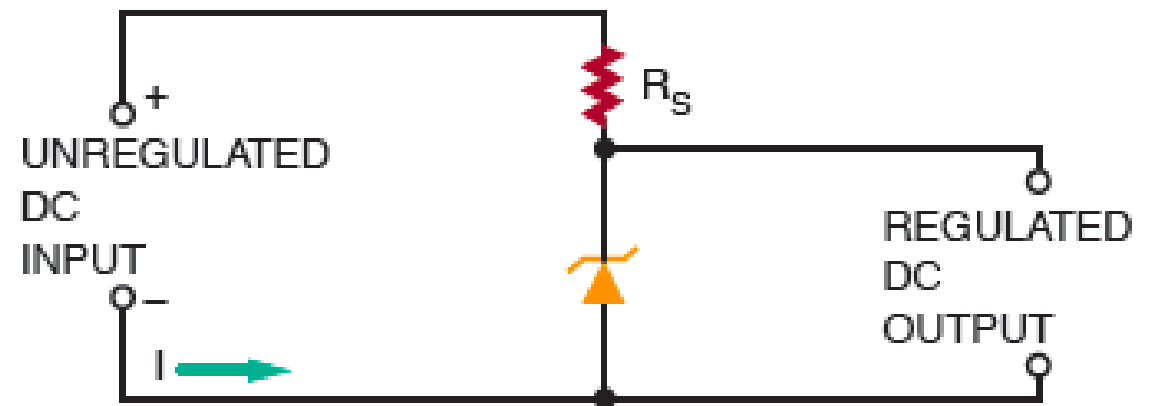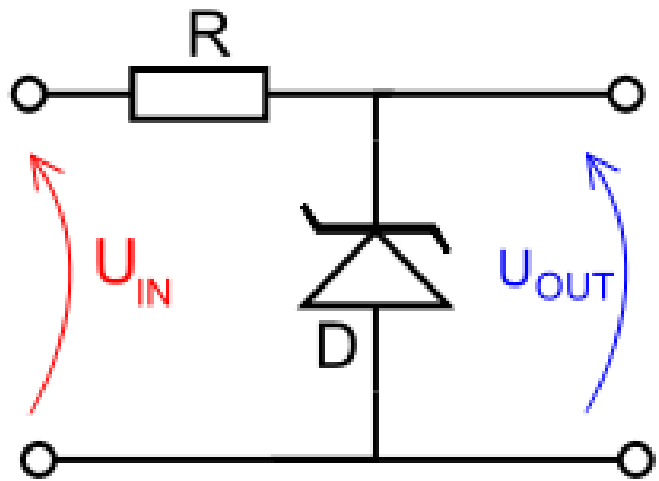- **Voltage regulation** is the most common application of a zener diode.
- Provides a constant output voltage despite changes in the input voltage or output current





Recall: Rectifier Output is a Bumpy Ride

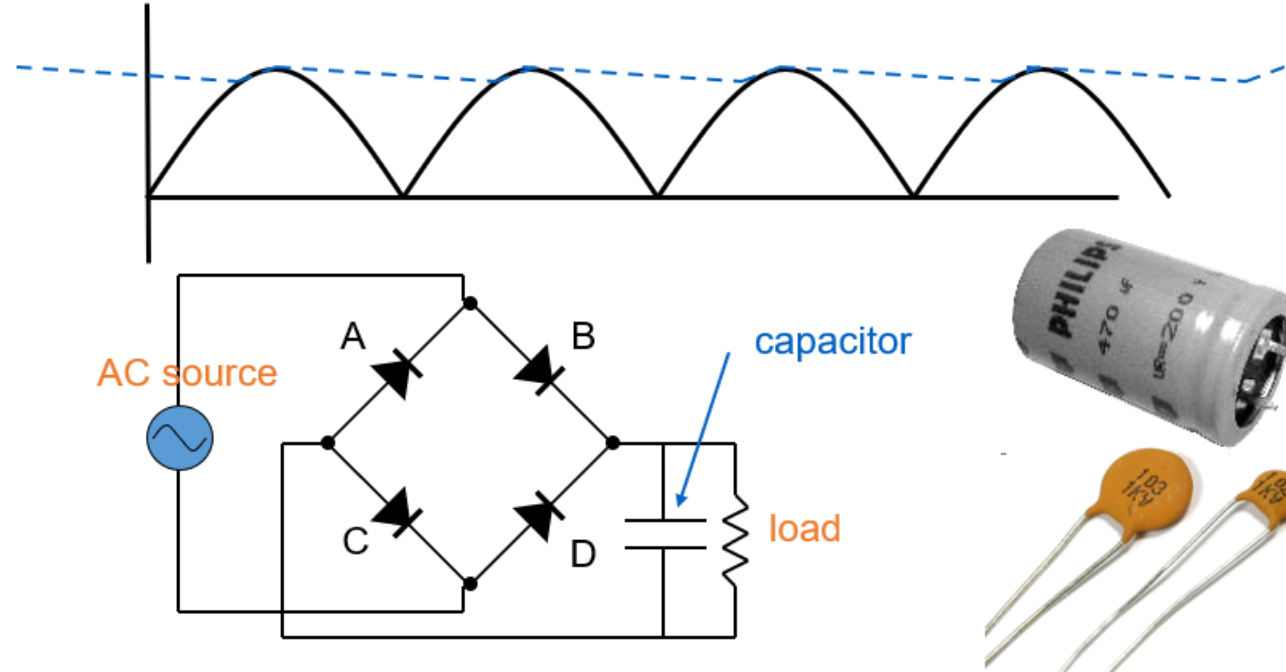- Rectifier uses a capacitor to smooth out pulses
 - capacitors have capacity for storing charge
 - acts like a **reservoir** to supply current during low spots
 - voltage regulator smoothers out remaining ripple




How smooth is smooth?

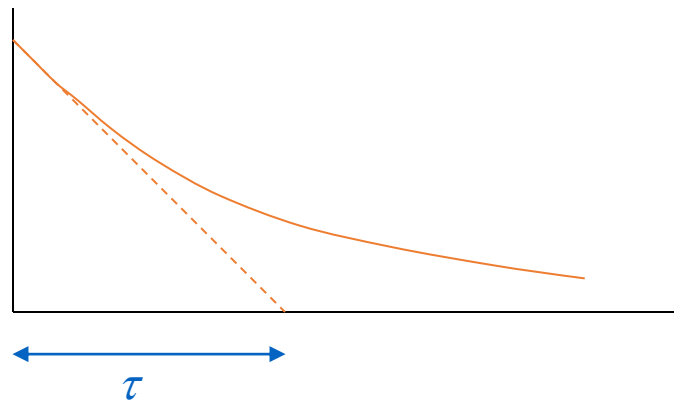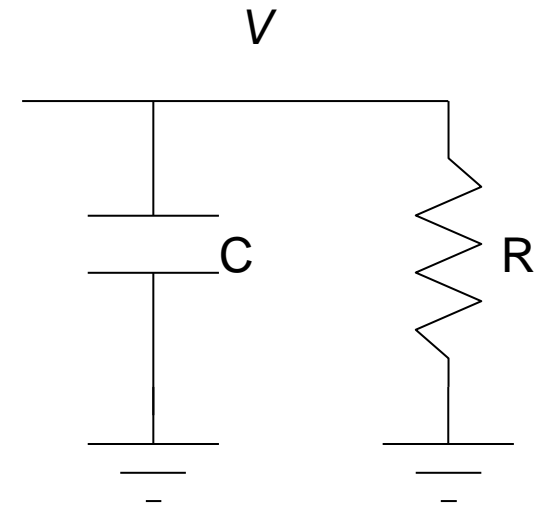- An RC circuit has a time constant $\tau = RC$
 - because $dV/dt = I/C$, and $I = V/R \rightarrow dV/dt = V/RC$
 - so V is $V_0 \exp(\pm t/\tau)$
- Any exponential function starts out with slope = Amplitude/ τ
- So if you want < 10% ripple over 120 Hz (8.3 ms) timescale...
 - must have $\tau = RC > 83$ ms
 - if $R = 100 \Omega$, $C > 830 \mu\text{F}$




Regulating the Voltage

- The **unregulated**, ripple voltage may not be at the value you want:
 - depends on transformer, etc.
 - suppose you want 15.0 V
- You *could* use a **voltage divider** to set the voltage.
- But it would **droop** (bend or hang downwards limply) under load
 - output impedance $\rightarrow R_1 \parallel R_2$
 - need to have very small R_1, R_2 to make it “stiff”
 - the divider will draw a lot of current
 - perhaps straining the source
 - power expended in divider \gg power in load
- Not a “real” solution
- **Important note:** a “big load” means a small resistor value: $1\ \Omega$ demands more current than $1\ \text{M}\Omega$

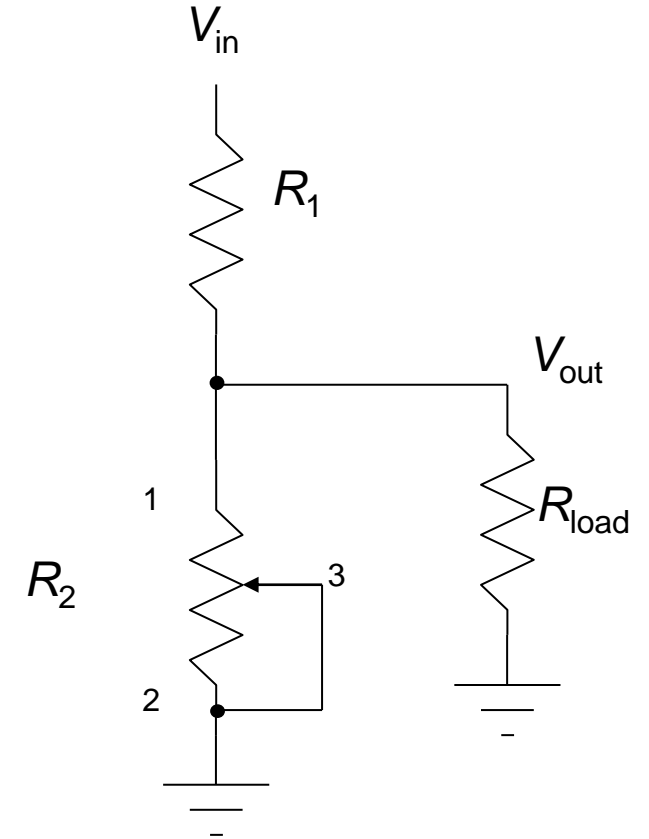


The Zener Regulator



- Zener diodes **break down** at some reverse voltage
 - can be at specific breakdown voltages
 - as long as **some** current goes through zener, it'll work
- Conditions for working:
 - let's maintain some minimal current, I_z through zener (say a few mA)
 - then $(V_{in} - V_{out})/R_1 = I_z + V_{out}/R_{load}$ sets the requirement on R_1 because presumably all else is known
 - if load current increases too much, zener shuts off (node drops below breakdown) and you just have a voltage divider with the load

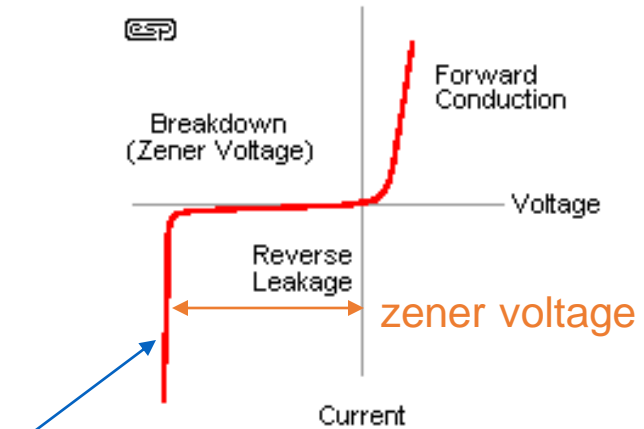

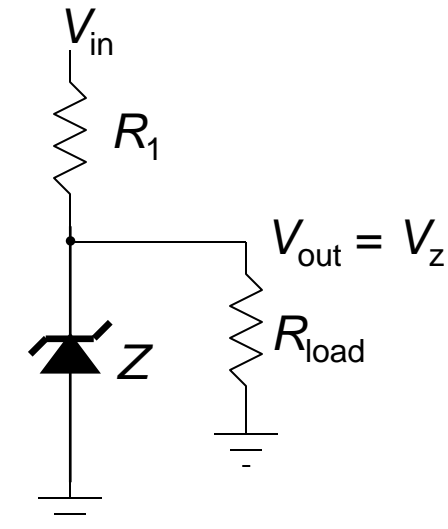
high slope is what makes the zener a decent voltage regulator




Reverse Bias in
Volts

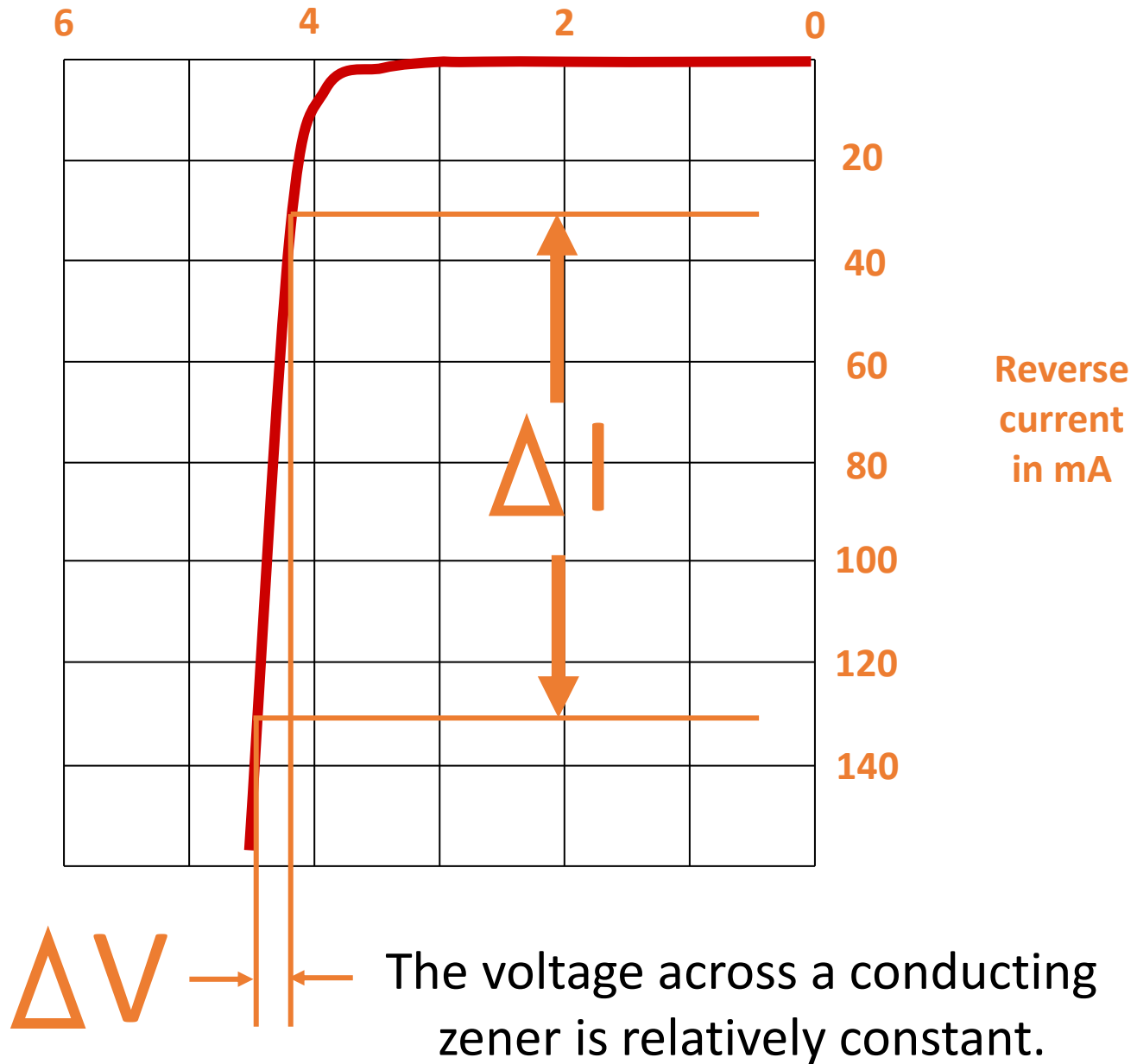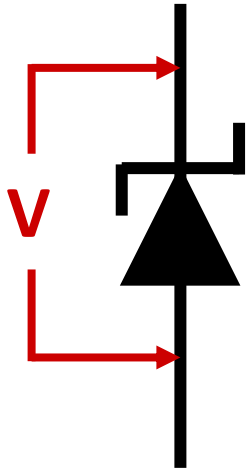

Zener as Regulator

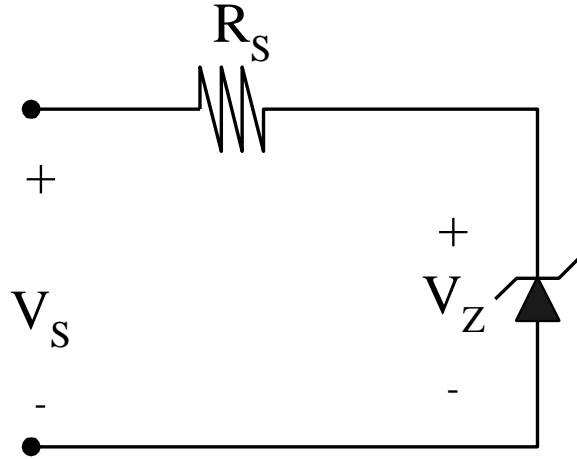


A simple regulator circuit

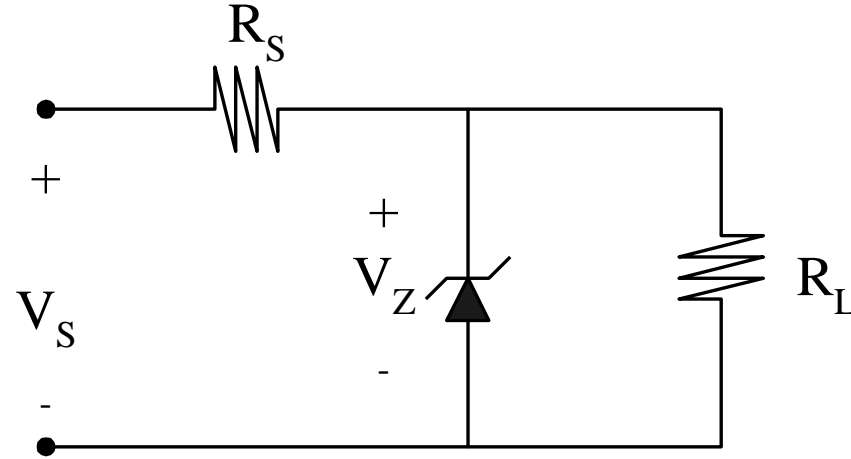


A regulator circuit with load resistance

- R_S is to limit the zener current, I_Z so that it is less than the maximum current, I_{ZM} (to avoid the zener diode from broken).
- How to determine whether the zener acts as a regulator or not??
 - Use Thevenin Theorem

Thevenin Equivalent Circuit

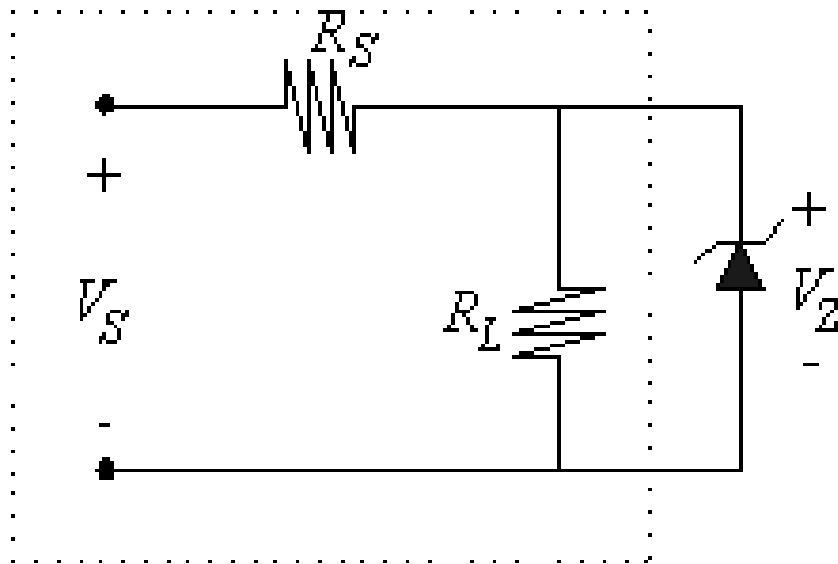

(a)

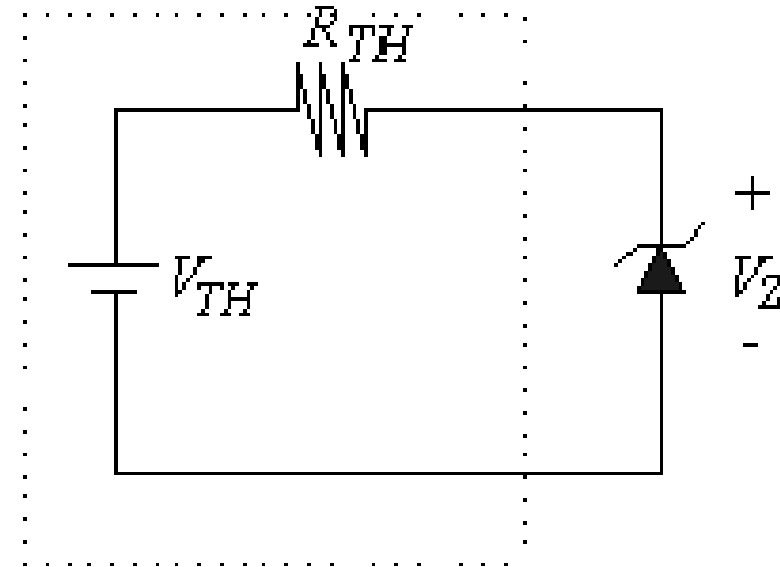



(b)

- If $V_{TH} < V_Z$, regulation does not occur.

Zener I-V Characteristic


- In the zener **I-V characteristic curve**, if the voltage across the zener diode is between **0- V_Z** , the zener diode is operating in the **reverse bias region**, thus it **DOES NOT** functioned as a regulator.
- V_{TH} must **at least** the **same value as V_Z** ($V_{TH} \geq V_Z$) so that the diode **CAN** function as a voltage regulator because it is operating in **reverse breakdown region**.

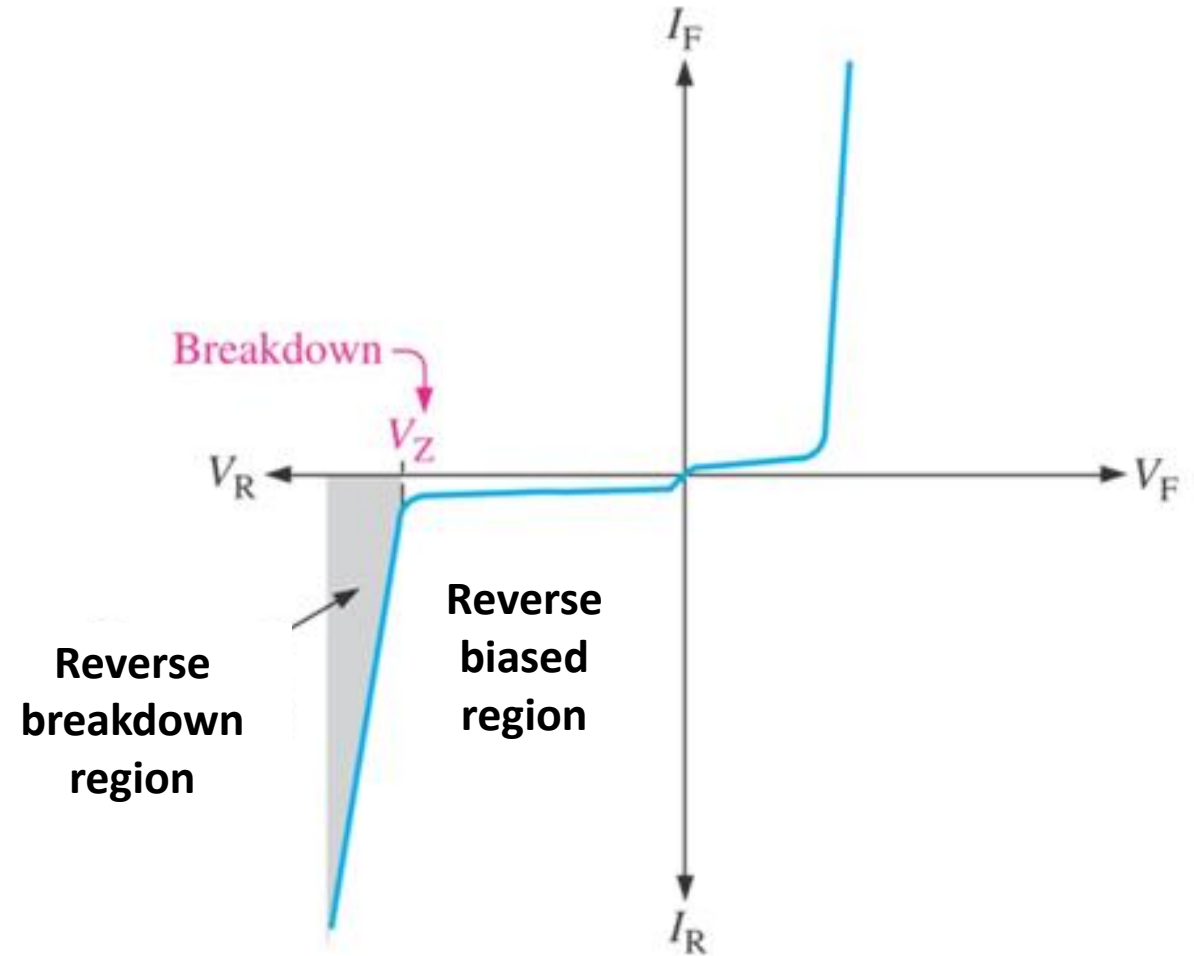

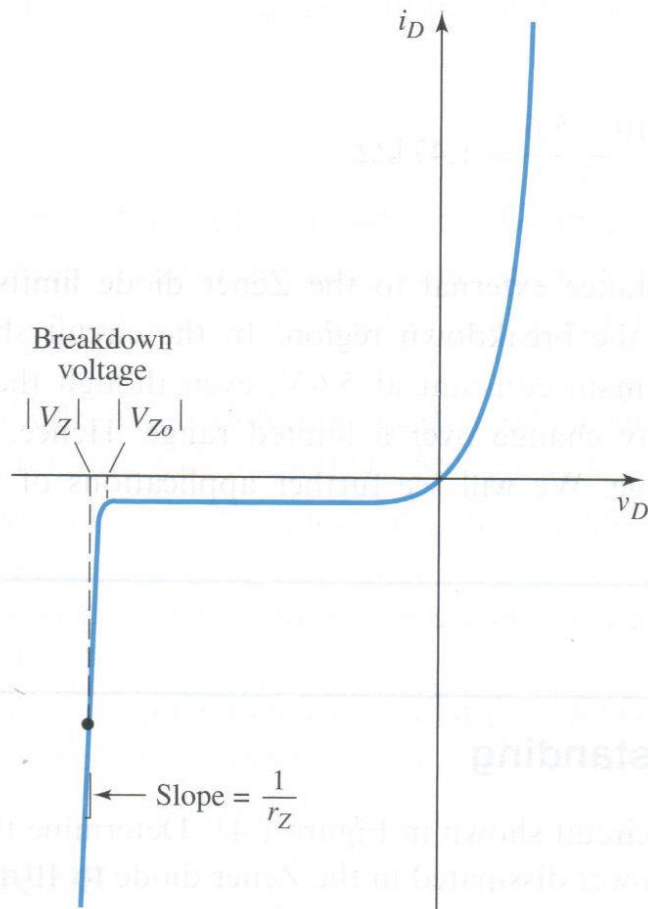

- The breakdown voltage of a Zener diode is nearly constant over a wide range of reverse-bias currents.
- This makes the Zener diode useful in a **voltage regulator**, or a constant-voltage reference circuit.

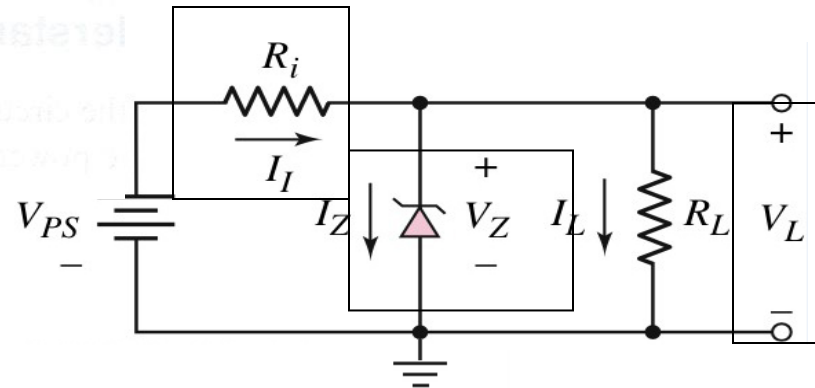3. The remainder of V_{PS} drops across R_i



2. The load resistor sees a constant voltage regardless of the current

1. The zener diode holds the voltage constant regardless of the current

Zener Analysis


- Three types of Zener analysis
 - Fixed V_S and R_L
 - Fixed V_S and variable R_L
 - Variable V_S and fixed R_L

Fixed V_S and R_L

The applied dc voltage is fixed, as the load resistor.

The analysis :

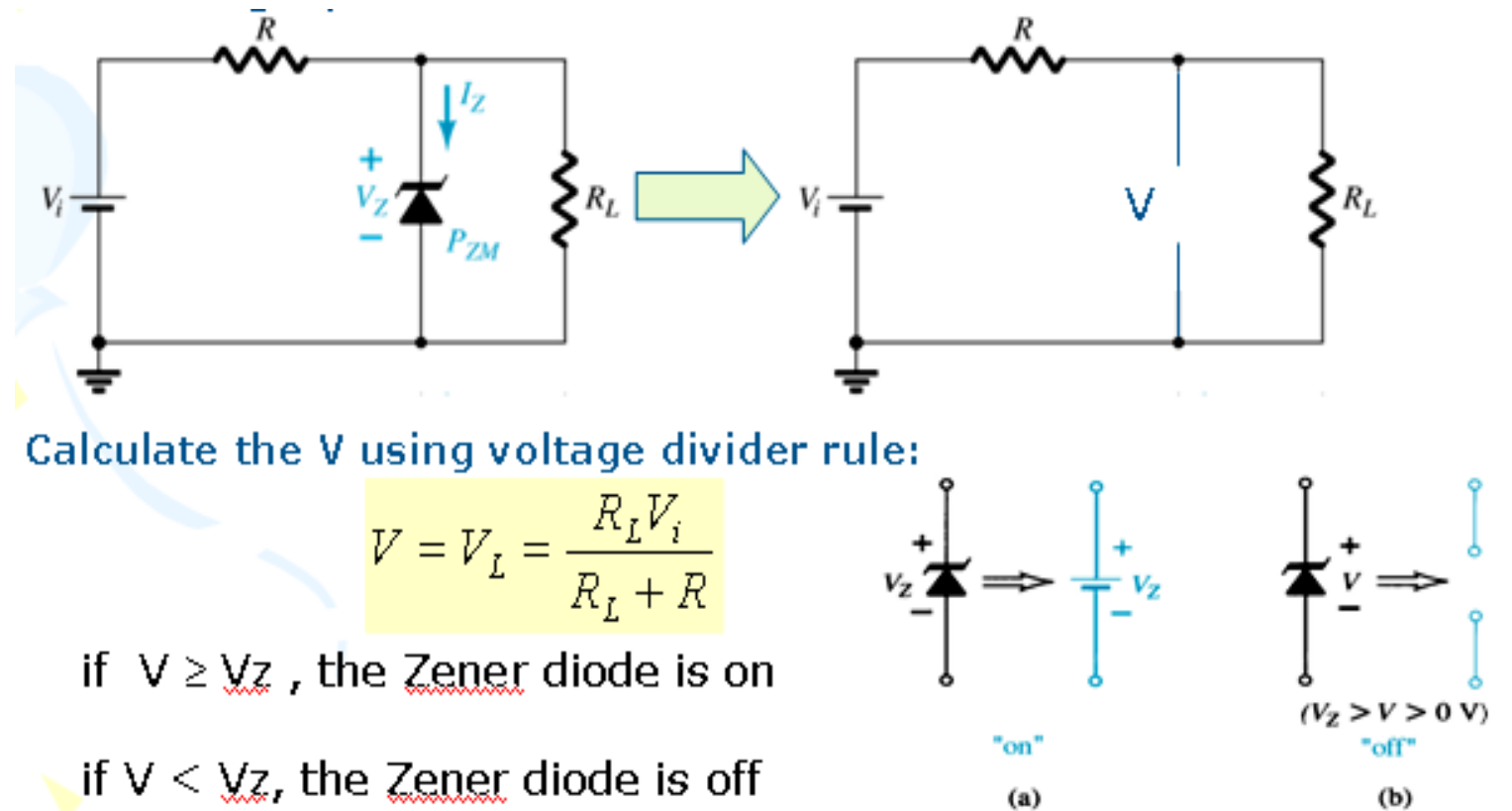1. Determine the state of the Zener diode by **removing it** from the network and **calculating the voltage** across the resulting open circuit.



2. Substitute the appropriate equivalent circuit and solve for the desired unknowns.

- For the **on state diode**, the voltages across parallel elements must be the same.

$$V_L = V_Z$$

The Zener diode current is determined by KCL:


$$I_Z = I_R - I_L$$

The power dissipated by the Zener diode is determined by:

$$P_Z = V_Z I_Z$$

- For the **off state diode**, the equivalent circuit is open-circuit.

Fixed V_S and Variable R_L

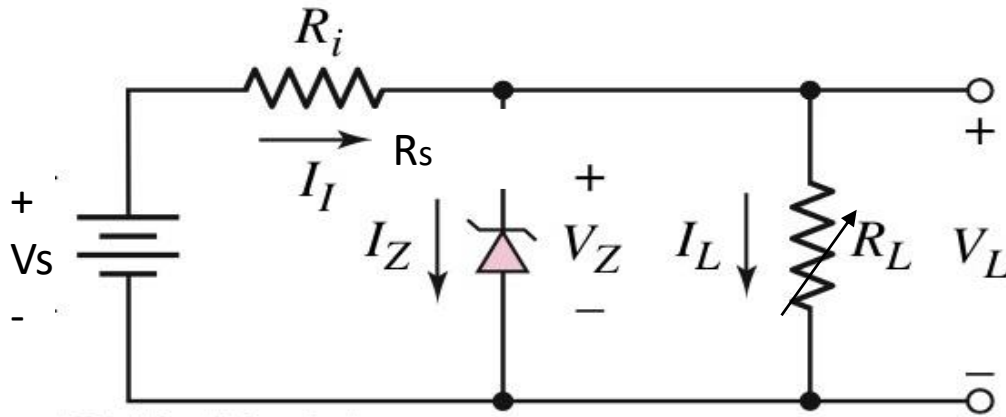

ht © The McGraw-Hill Companies, Inc.
ion required for reproduction or display.

Step 1- get the R_{Lmin} so that zener is on.

$$V_L = \frac{R_L V_S}{R_S + R_L} \longrightarrow R_{Lmin} = \frac{R_S V_Z}{V_S - V_Z}$$

- if $R_L \geq R_{Lmin}$, zener diode 'on', so that $V_L = V_Z$

Step 2: Calculate the I_Z using KCL: 2 condition

1. If R_{Lmin} , then I_{Lmax} and I_{Zmin} because of constant I_1
2. If R_{Lmax} , then I_{Lmin} and I_{Zmax}


$$I_{Z \min \text{ or max}} = I_{1 \text{ constant}} - I_{L \max \text{ or min}} \quad ; \text{ Izmax taken from data sheet}$$

Izmin = 0, if not given

Where

$$I_1 = \frac{V_S - V_Z}{R_S} \quad \text{and} \quad I_{L \max} = \frac{V_Z}{R_{L \min}} \quad \text{or} \quad R_{L \max} = \frac{V_Z}{I_{L \min}}$$

Variable V_S and fixed R_L

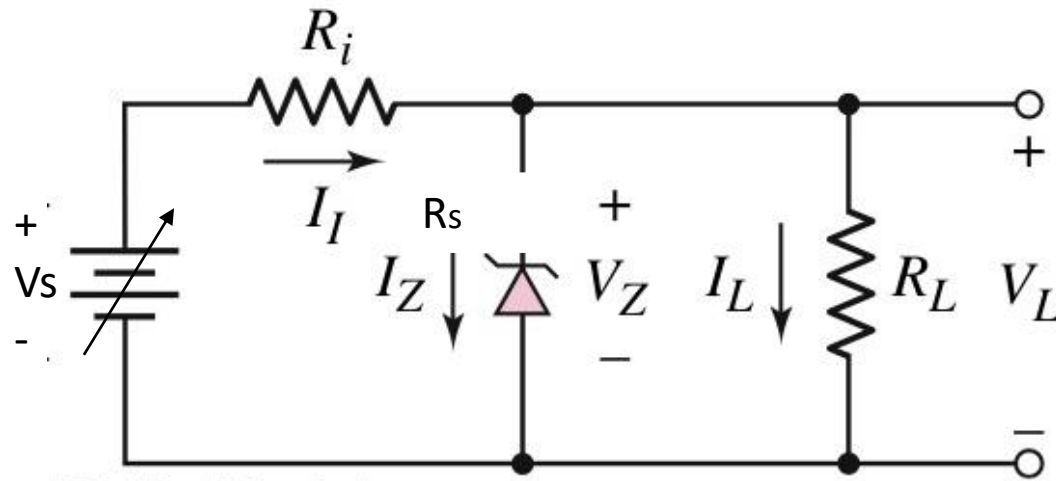

ht © The McGraw-Hill Companies, Inc.
ion required for reproduction or display.

Step 1- get the V_{Smin} so that zener is on.

$$V_L = \frac{R_L V_S}{R_S + R_L} \longrightarrow V_{Smin} = \frac{(R_L + R_S)V_Z}{R_L}$$

if $V_S \geq V_{Smin}$, zener diode will 'on',
so that $V_L = V_Z$

Step 2: Calculate the I_Z using KCL: 2 condition


1. if V_{Smin} , then I_{1min} and I_{Zmin} because of constant I_L
2. if V_{Smax} , then I_{1max} and I_{Zmax}

$$I_{Z \min \text{ or } \max} = I_{1 \min \text{ or } \max} - I_{L \text{ constant}} \quad ; I_{z \max} = P_{z \max} / V_z$$


$$\text{where } I_L = \frac{V_L}{R_L} \quad \text{and} \quad I_{1 \min} = \frac{V_{S \min} - V_Z}{R_S} \quad \text{or} \quad V_{S \max} = I_{1 \max} R_S + V_Z$$

Zener Regulation Circuit

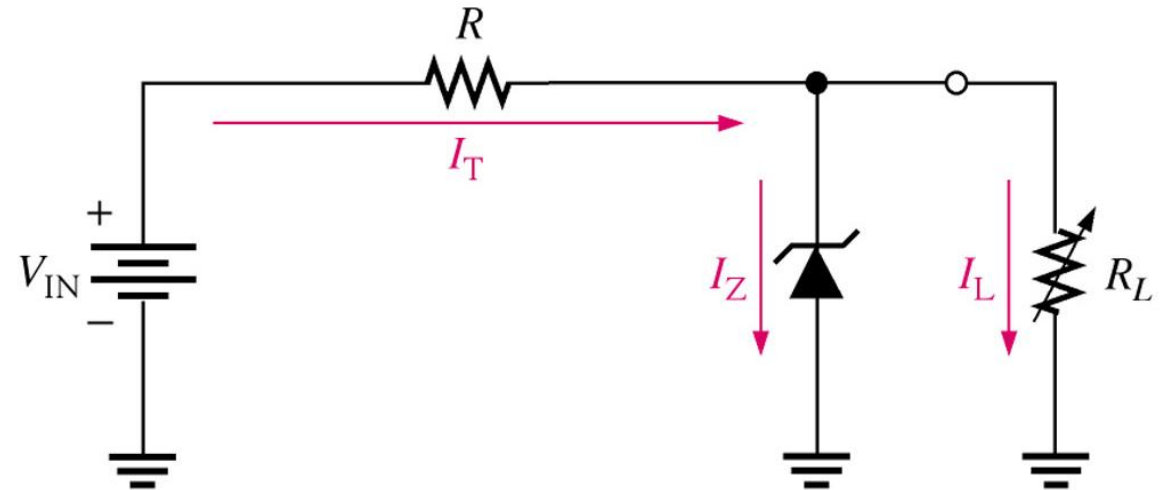
- The zener diode will “adjust” its impedance based on varying input voltages and loads (R_L) to be able to maintain its designated zener voltage.
- Zener current will increase or decrease directly with voltage input changes.
- The zener current will increase or decrease inversely with varying loads.
- Again, the zener diode has a finite range of operation.



Zener Diode as Voltage Regulator

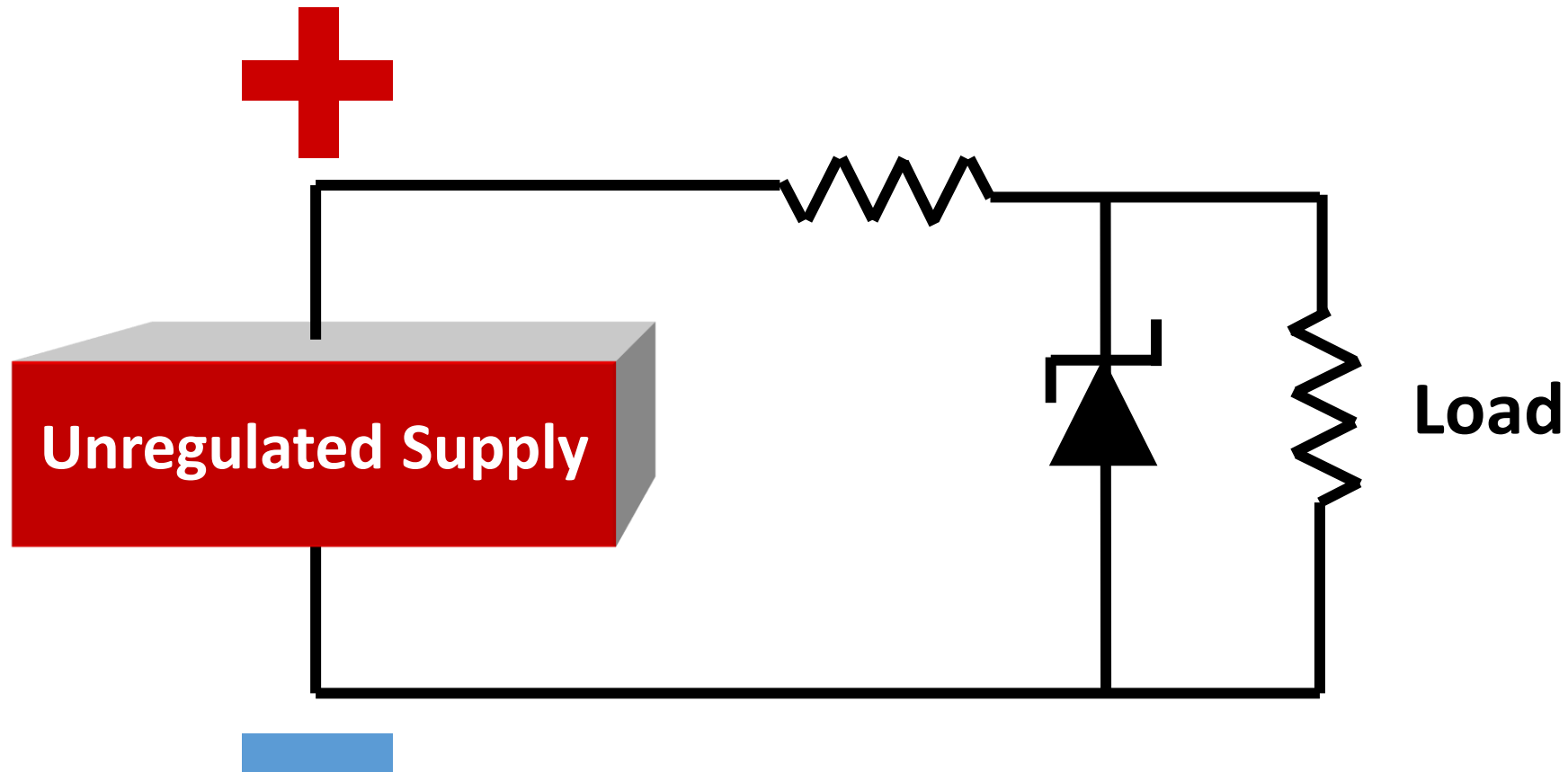


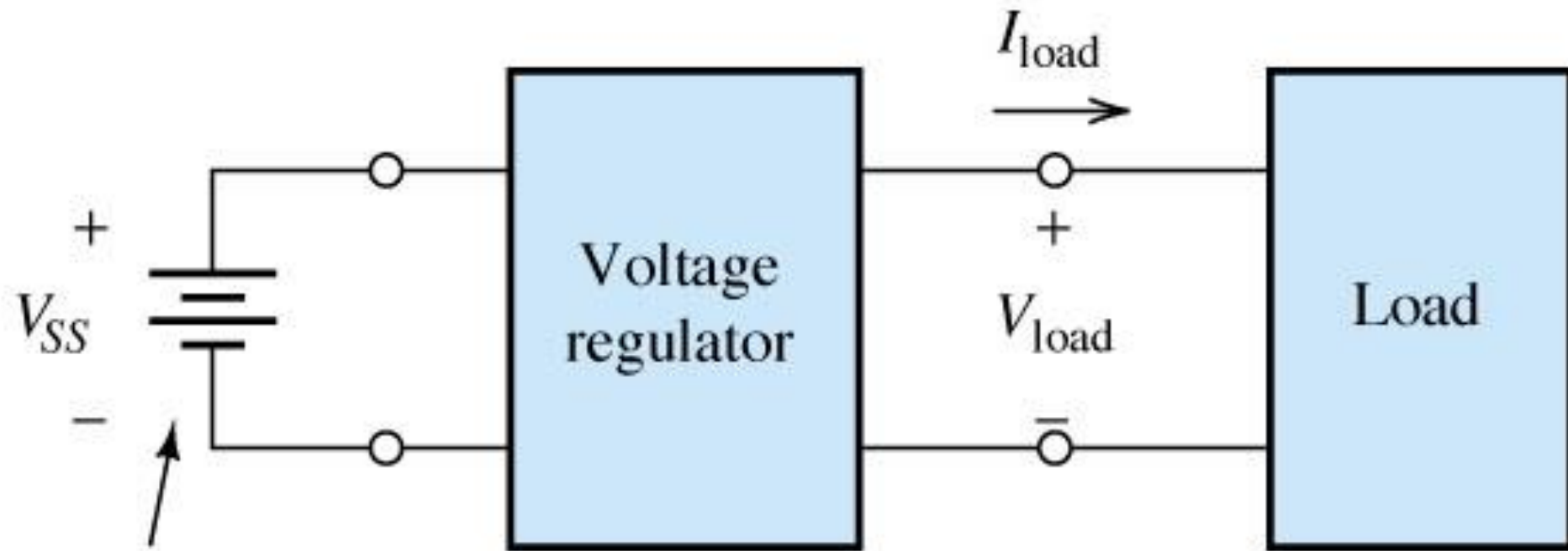The load is in parallel with the zener and will see a relatively constant voltage as long as the zener is conducting.




Variable source

Example 1

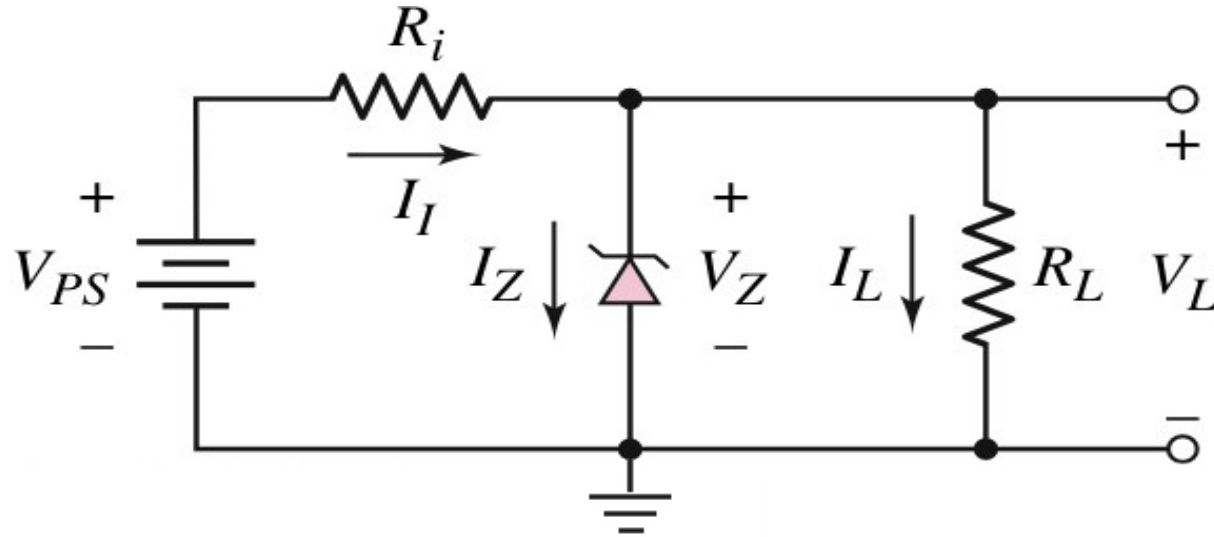

A Zener diode is connected in a voltage regulator circuit. It is given that $V_{PS} = 20\text{V}$, the Zener voltage, $V_Z = 10\text{V}$, $R_i = 222\ \Omega$ and $P_{Z(\text{max})} = 400\text{ mW}$.

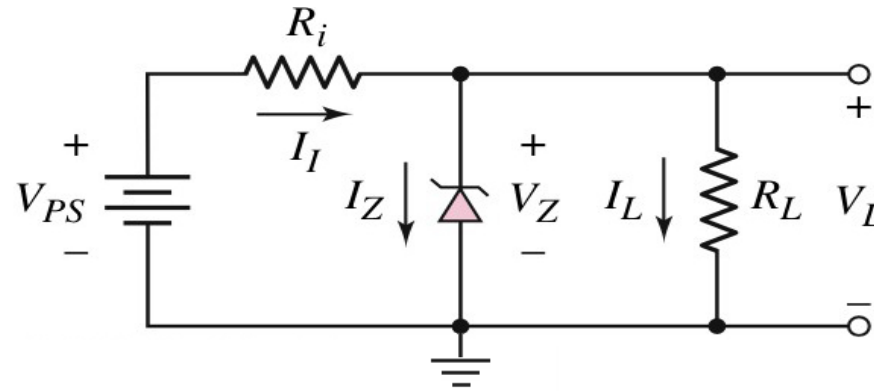- Determine the values of I_L , I_Z and I_i if $R_L = 380\ \Omega$.
- Determine the value of R_L that will establish $P_{Z(\text{max})} = 400\text{ mW}$ in the diode.



For proper function the circuit must satisfy the following conditions.

1. The **power dissipation in the Zener diode** is less than the rated value
2. When the power supply is a minimum, $V_{PS}(\text{min})$, there must be minimum current in the zener diode $I_Z(\text{min})$, hence the load current is a maximum, $I_L(\text{max})$,
3. When the power supply is a maximum, $V_{PS}(\text{max})$, the current in the diode is a maximum, $I_Z(\text{max})$, hence the load current is a minimum, $I_L(\text{min})$

$$R_i = \frac{V_{PS}(\text{min}) - V_Z}{I_Z(\text{min}) + I_L(\text{max})} \quad \text{AND} \quad R_i = \frac{V_{PS}(\text{max}) - V_Z}{I_Z(\text{max}) + I_L(\text{min})} \quad \text{Or, we can write}$$

$$[V_{PS}(\text{min}) - V_Z] \cdot [I_Z(\text{max}) + I_L(\text{min})] = [V_{PS}(\text{max}) - V_Z] \cdot [I_Z(\text{min}) + I_L(\text{max})]$$

For general thumb of rule for design this circuit is, so from the last Equation


$$I_Z(\text{max}) = \frac{I_L(\text{max}).[V_{PS}(\text{max}) - V_Z] - I_L(\text{min}).[V_{PS}(\text{min}) - V_Z]}{V_{PS}(\text{min}) - 0.9V_Z - 0.1V_{PS}(\text{max})}$$

Maximum power dissipation in the Zener diode is

$$P_Z(\text{max}) = I_Z(\text{max}) \times V_Z$$

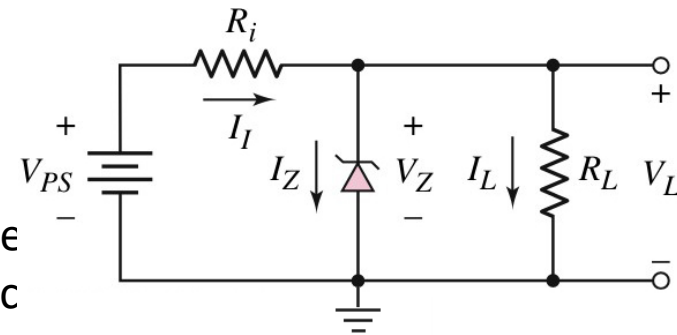EXAMPLE


Consider voltage regulator is used to power the ce phone at 2.5 V from the lithium ion battery, which voltage may vary between 3 and 3.6 V. The current in the phone will vary 0 (off) to 100 mA(when talking). Calculate the value of R_i and the Zener diode power dissipation



simple Zener diode voltage regulator circuit

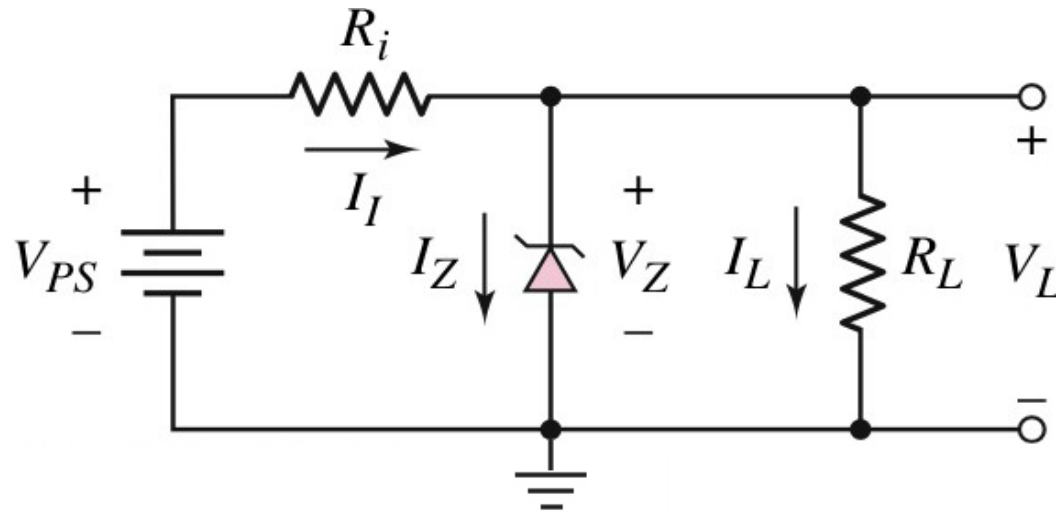Example 2

Consider voltage regulator is used to power the cell phone at 2.5 V from the lithium ion battery, which voltage may vary between 3 and 3.6 V. The current in the phone will vary 0 (off) to 100 mA(when talking). Calculate the value of R_i and the Zener diode power dissipation



Solution:

The stabilized voltage $V_L = 2.5$ V, so the Zener diode voltage must be $V_Z = 2.5$ V. The maximum Zener diode current is

$$I_Z(\text{max}) = \frac{I_L(\text{max}) \cdot [V_{PS}(\text{max}) - V_Z] - I_L(\text{min}) \cdot [V_{PS}(\text{min}) - V_Z]}{V_{PS}(\text{min}) - 0.9V_Z - 0.1V_{PS}(\text{max})}$$

$$\text{Or, } I_Z(\text{max}) = \frac{100 \times [3.6 - 2.5] - 0 \times [3 - 2.5]}{3 - 0.9 \times 2.5 - 0.1 \times 3.6} = 282.05 \text{ mA}$$

The maximum power dissipation in the Zener diode is $P_Z(\text{max}) = I_Z(\text{max}) \times V_Z = 282.05 \times 2.5 = 705.13 \text{ mW}$

The value of the current limiting resistance is

$$R_i = \frac{V_{PS}(\text{max}) - V_Z}{I_Z(\text{max}) + I_L(\text{min})} = \frac{3.6 - 2.5}{282.05 + 0} \approx 3.9 \Omega$$



References:

- Microelectronic Circuits, 7th edition by Adel S. Sedra Kenneth C. Smith.
- G. Streetman, and S. K. Banerjee, "Solid State Electronic Devices," 7th edition, Pearson, 2014.
- D. Neamen, D. Biswas, "Semiconductor Physics and Devices," McGraw-Hill Education.
- Electronic Devices and Circuit Theory 11th Edition by Boylestad, Robert . L, Louis Nashelskyl.
- <http://ecee.colorado.edu/~bart/book/book/contents.htm>
- <http://www.ecse.rpi.edu/~schubert/Course-ECSE-2210-Microelectronics-Technology-2010/>