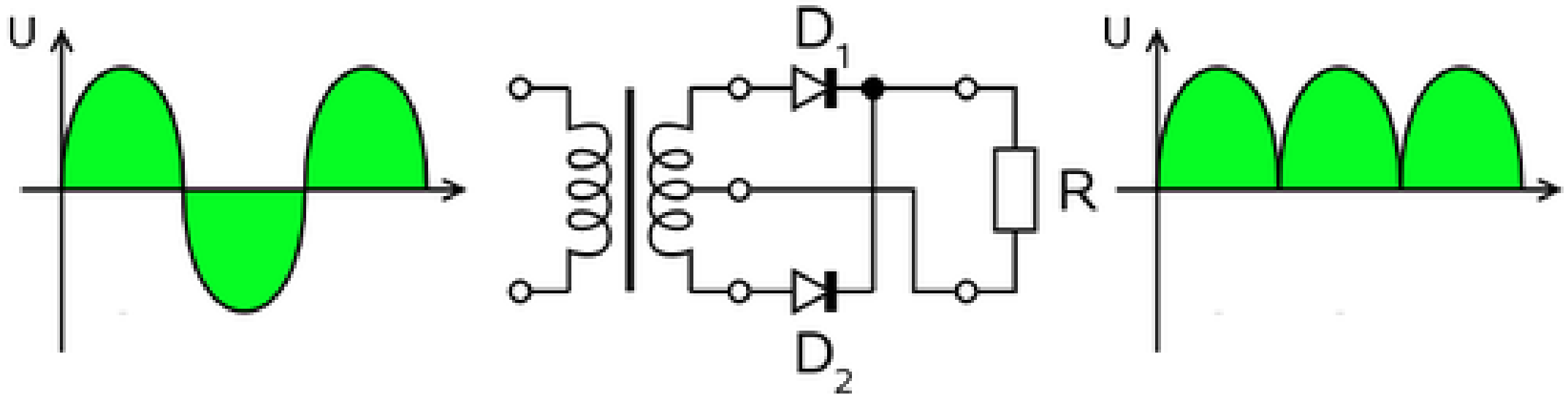


Full Wave Rectifier

Semiconductor Devices and Circuits
(ECE 181302)

12th November 2021

Full Wave Rectifier Using Transformer and 2 Diodes




Full-Wave Rectification with Center-Tapped Transformer


- *Positive cycle, D2 off, D1 conducts;*

$$V_o - V_s + V_\gamma = 0$$

$$\mathbf{V_o = V_s - V_\gamma}$$

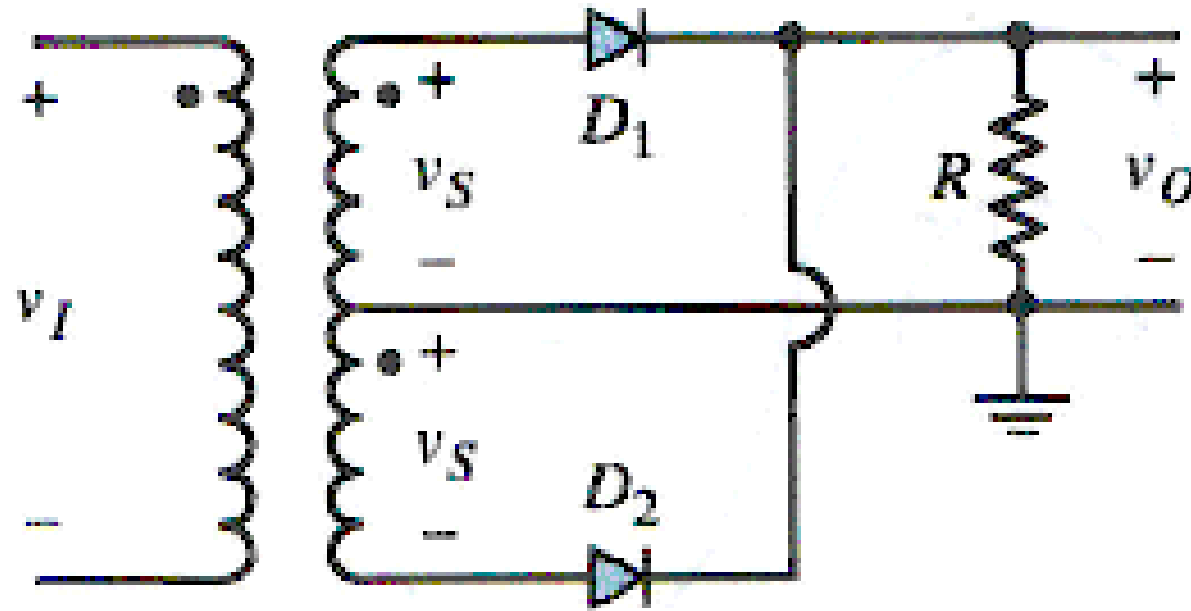

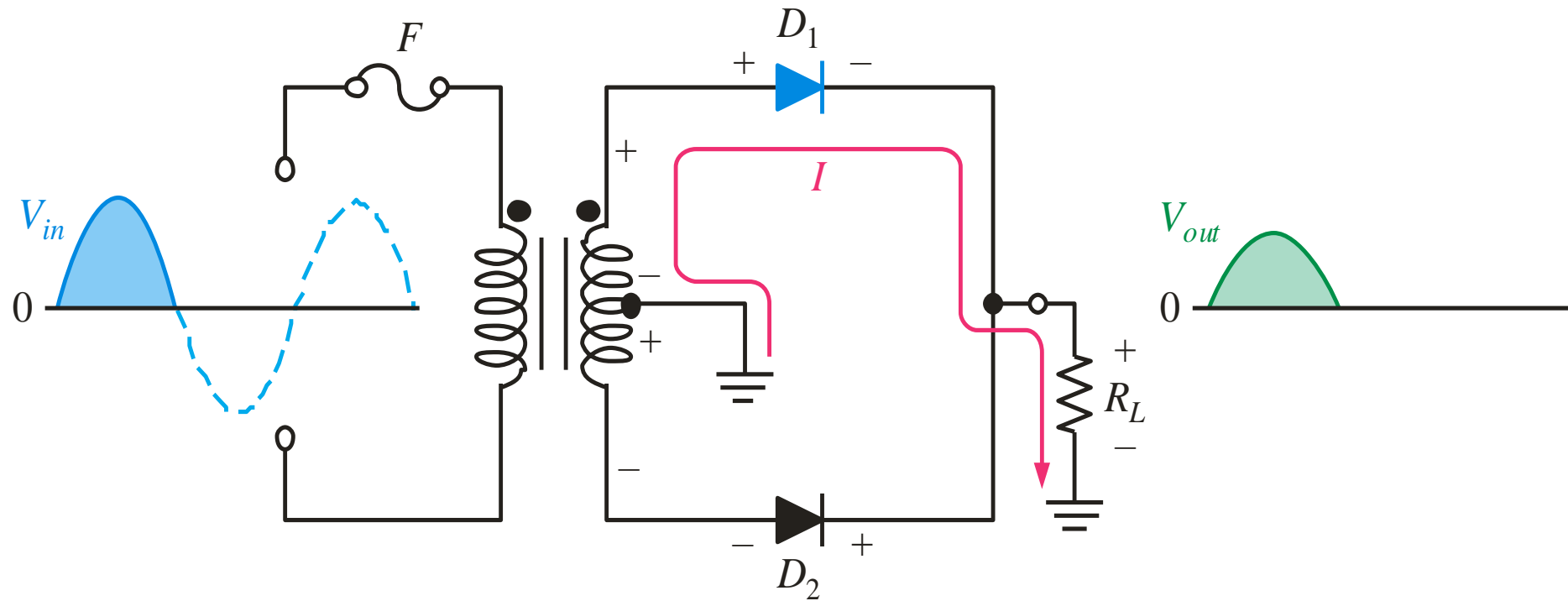During the positive half-cycle, the upper diode is forward-biased and the lower diode is reverse-biased.




Full-Wave Rectification with Center-Tapped Transformer


➤ *Negative cycle, D1 off, D2 conducts;*

$$V_o - V_s + V_\gamma = 0$$

$$V_o = V_s - V_\gamma$$

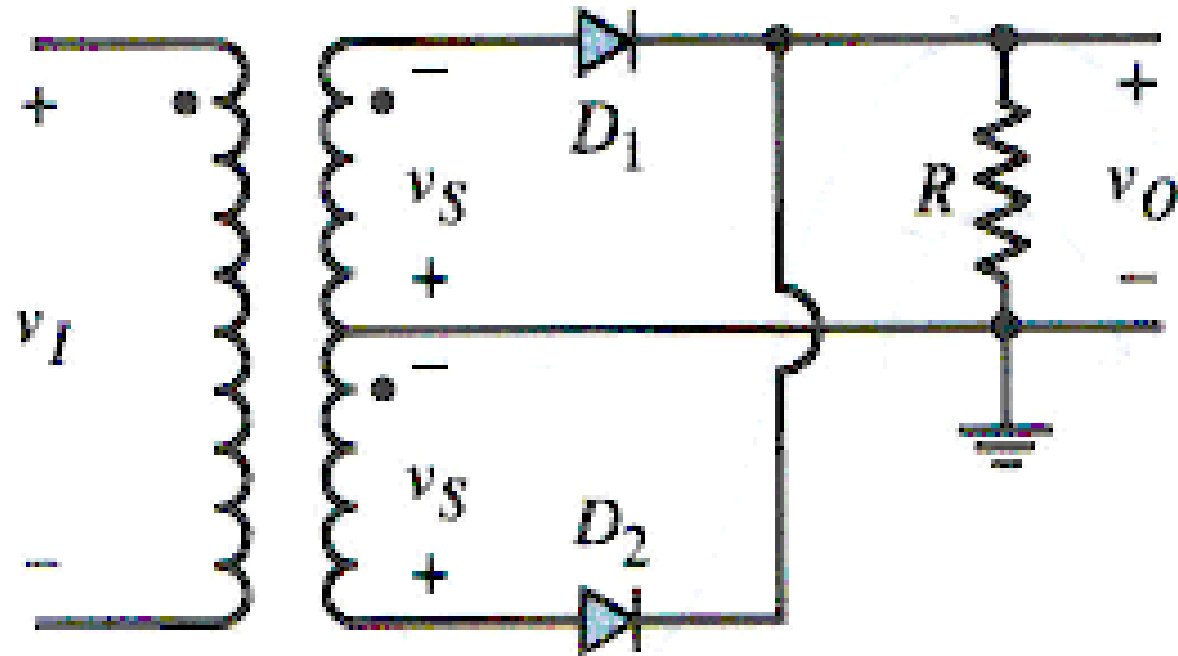

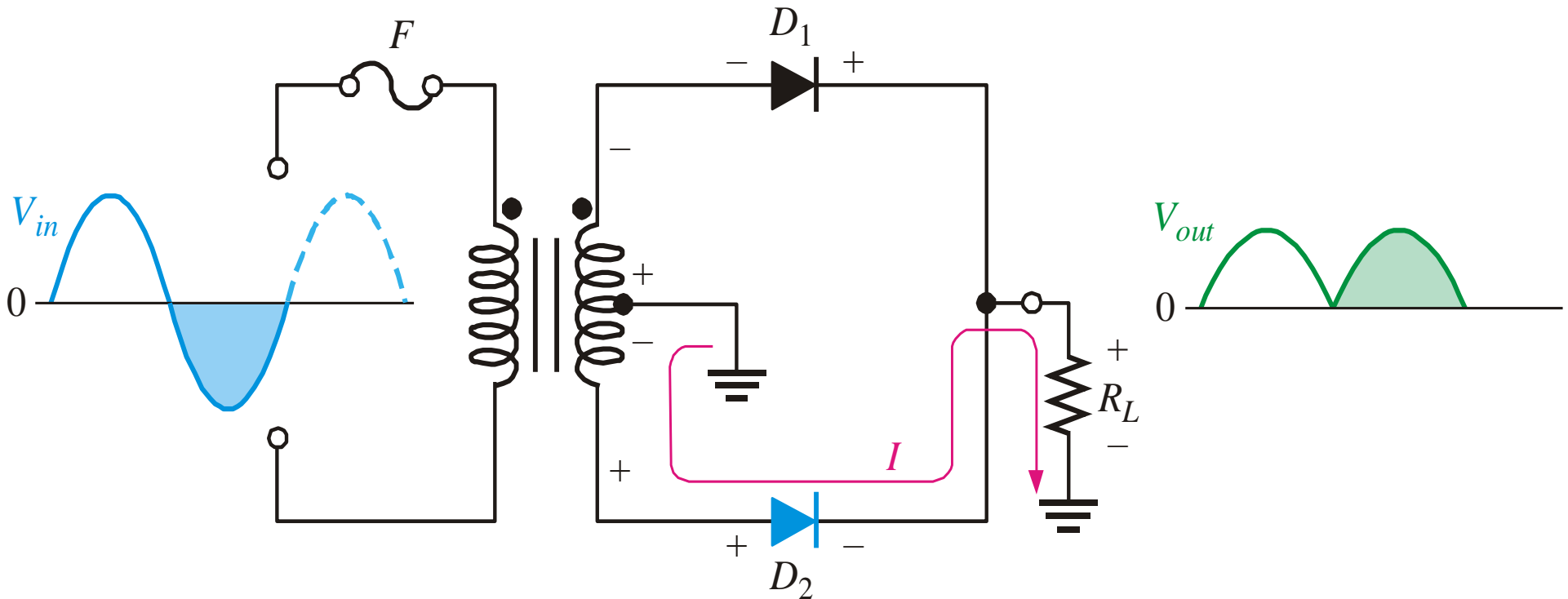During the negative half-cycle, the lower diode is forward-biased and the upper diode is reverse-biased.



- *Positive cycle*, D2 off, D1 conducts;

$$V_o - V_s + V_\gamma = 0$$



$$V_o = V_s - V_\gamma$$

- *Negative cycle*, D1 off, D2 conducts;


$$V_o - V_s + V_\gamma = 0$$

$$V_o = V_s - V_\gamma$$

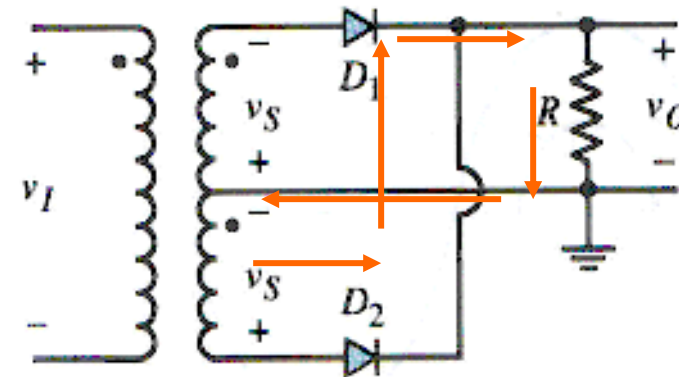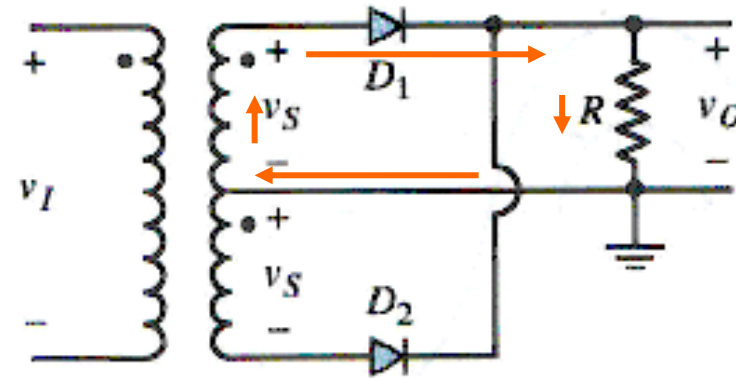- Since a rectified output voltage occurs during both positive and negative cycles of the input signal, this circuit is called a **full-wave rectifier**.
- Also notice that the **polarity of the output voltage for both cycles is the same**



$$V_s = V_p \sin \omega t$$

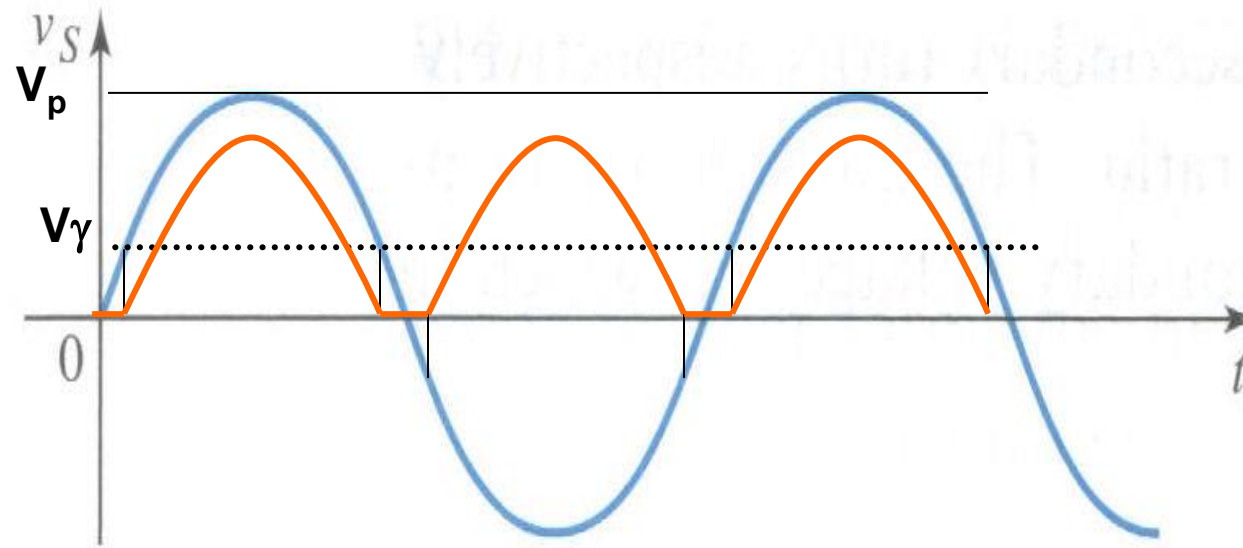



- Notice that the peak voltage of V_o is lower since **$V_o = V_s - V_\gamma$**
- **$V_s < V_\gamma$** , diode off, **open circuit**, no current flow, **$V_o = 0V$**

Full-Wave Rectification with Bridge Rectifier


- **Positive cycle**, D_1 and D_2 conducts, D_3 and D_4 off;

$$+ V_\gamma + V_O + V_\gamma - V_S = 0$$

$$\underline{V_O = V_S - 2V_\gamma}$$

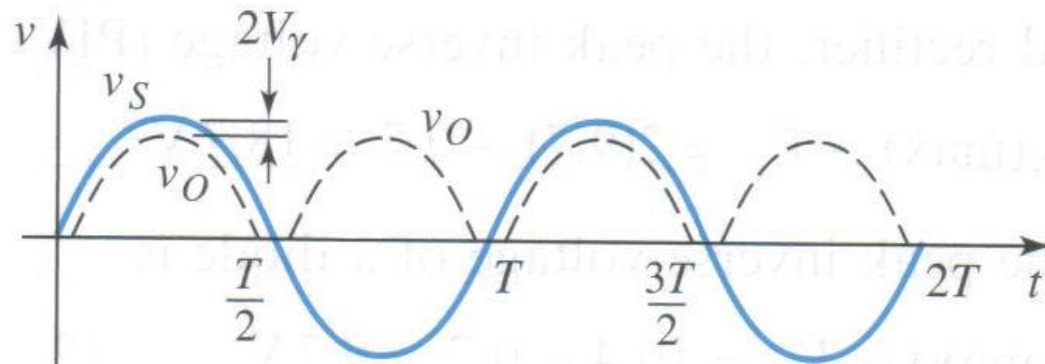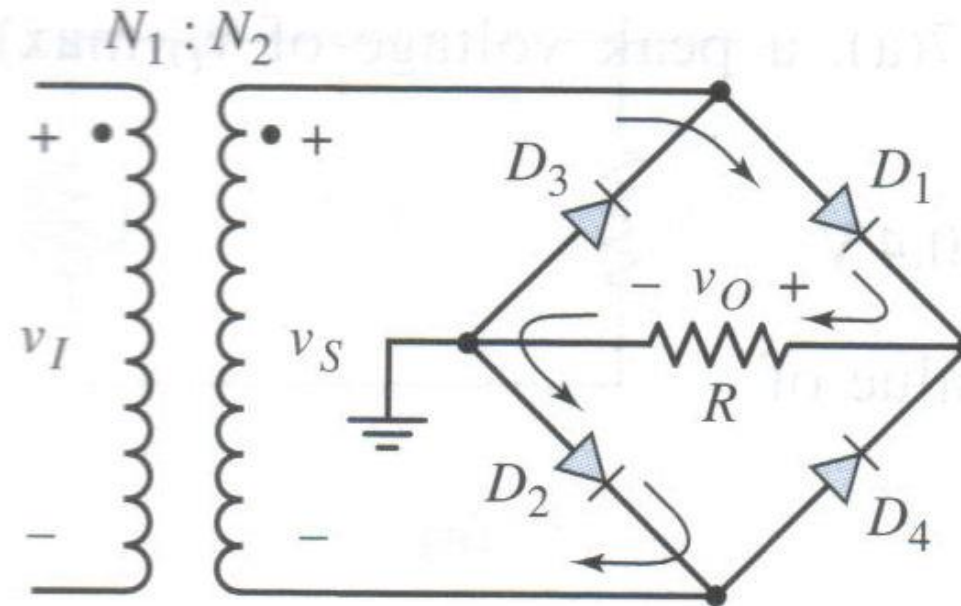

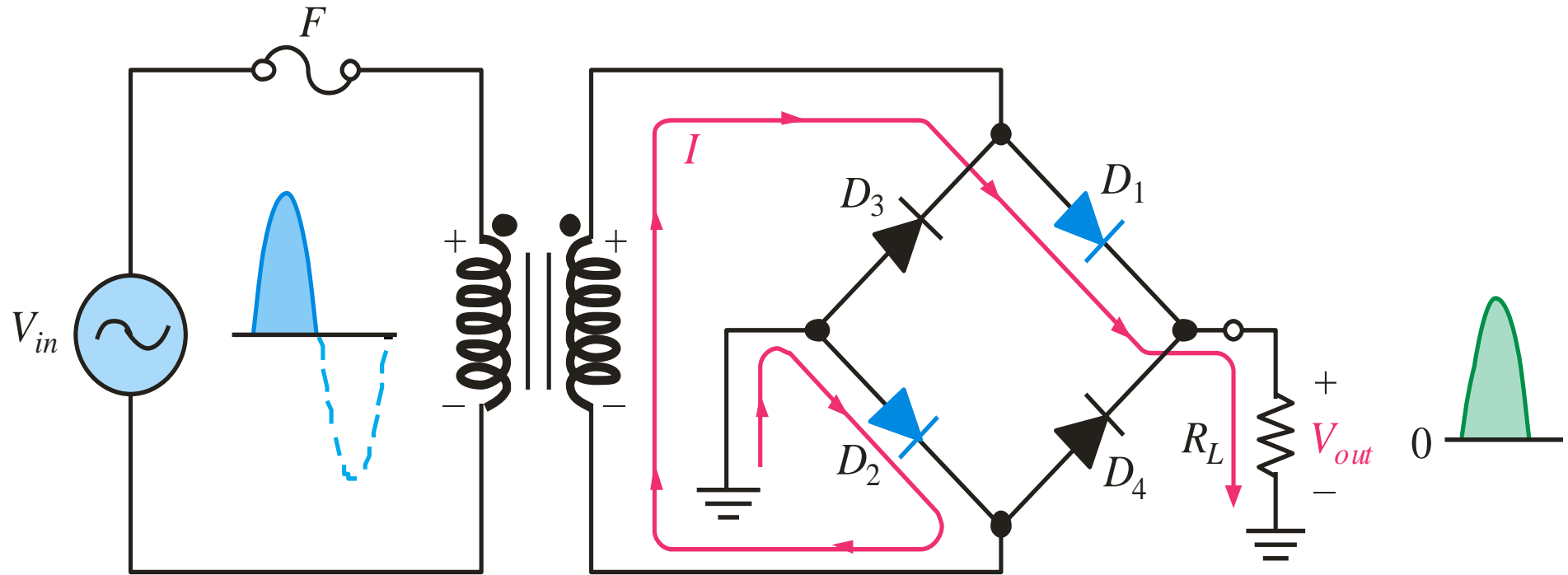Conduction path for the positive half-cycle.





Full-Wave Rectification with Bridge Rectifier


- **Negative cycle**, D_3 and D_4 conducts, D_1 and D_2 off

$$+V_\gamma + V_O + V_\gamma - V_S = 0$$


$$\underline{V_O = V_S - 2V_\gamma}$$

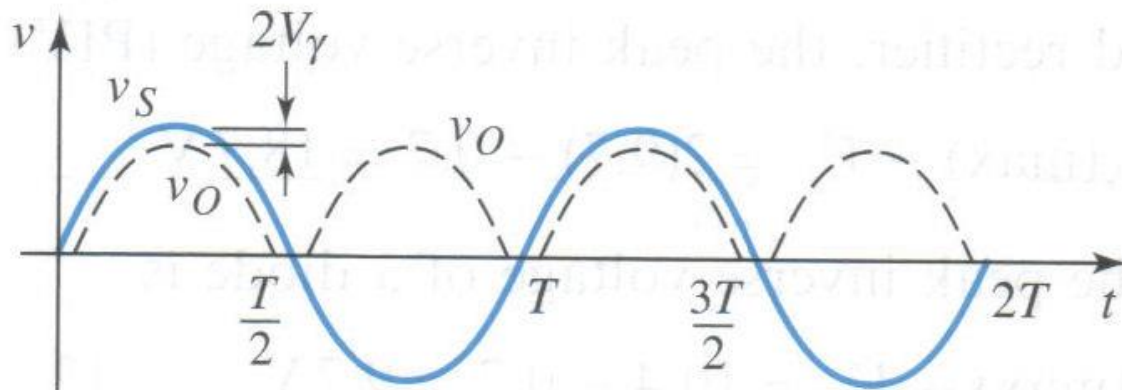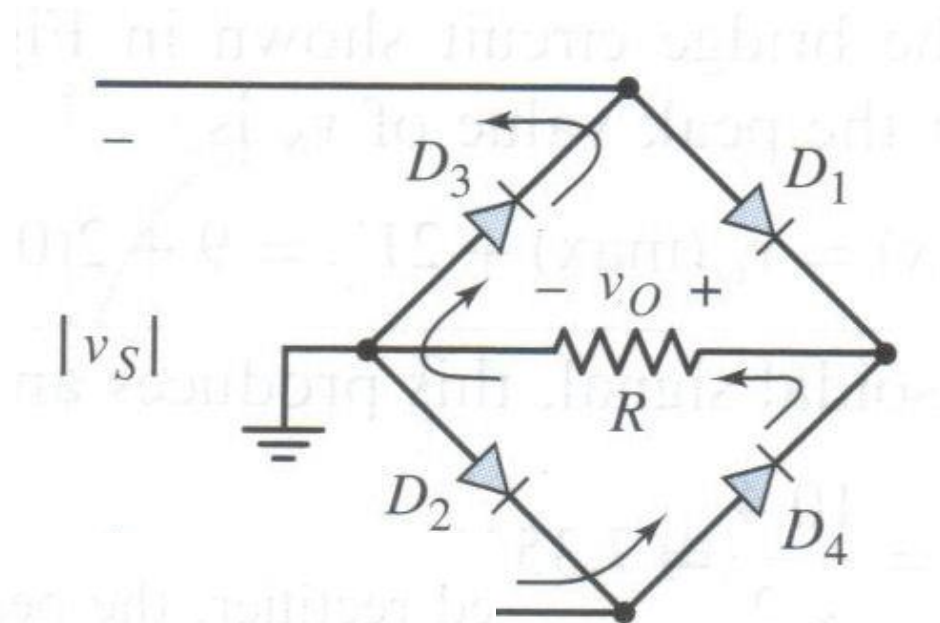

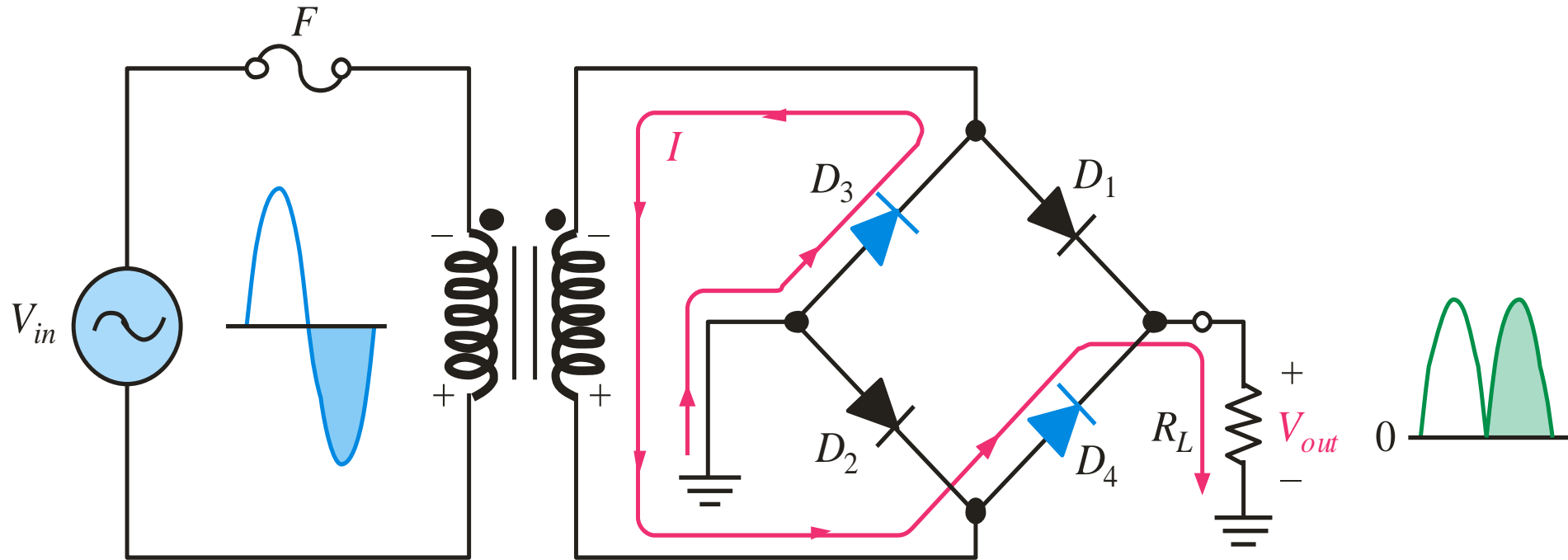Conduction path for the negative half-cycle.



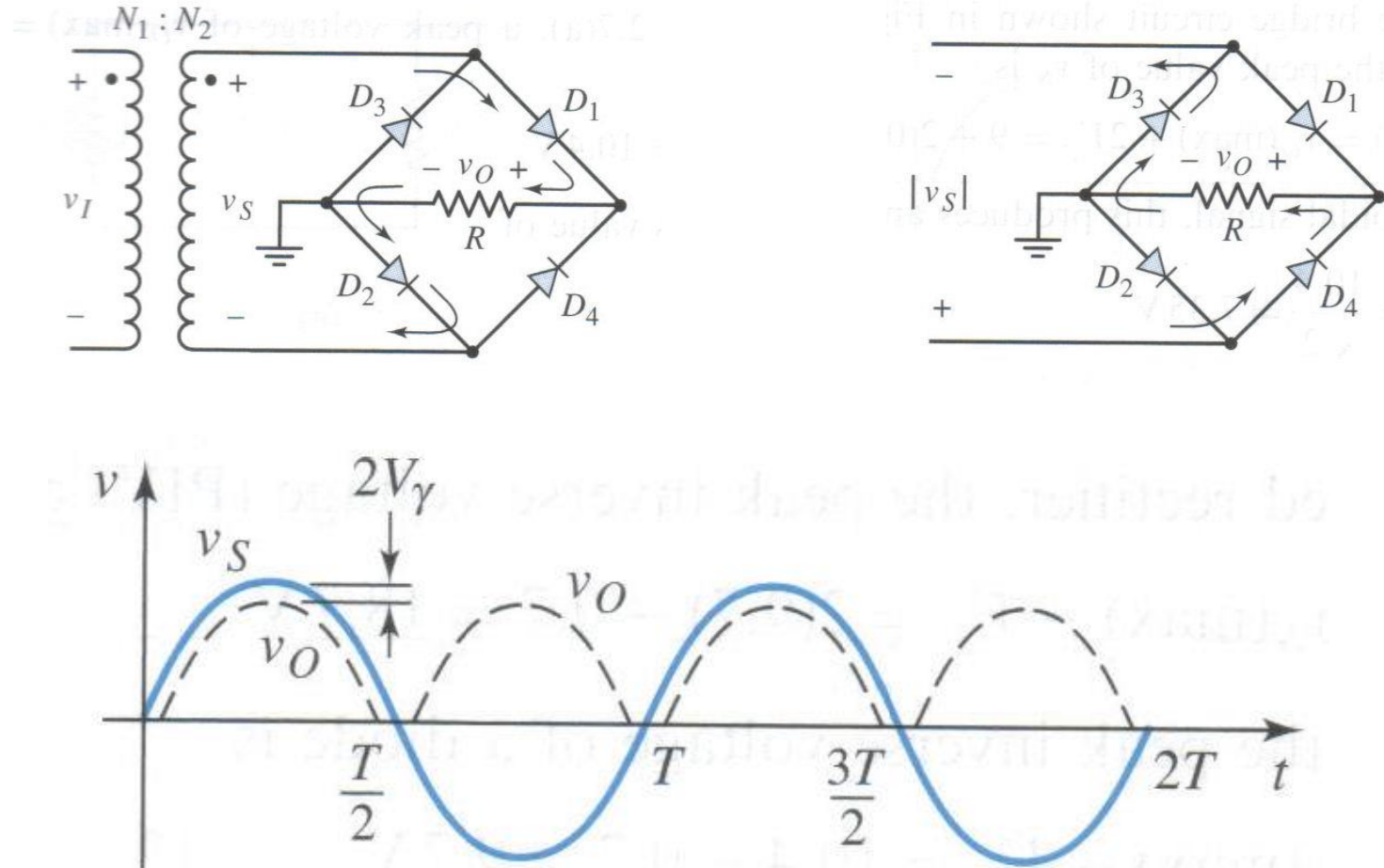Full-Wave Rectification with Bridge Rectifier



➤ Also notice that the **polarity of the output voltage for both cycles is the same**



References:

- Microelectronic Circuits, 7th edition by Adel S. Sedra Kenneth C. Smith.
- G. Streetman, and S. K. Banerjee, "Solid State Electronic Devices," 7th edition, Pearson, 2014.
- D. Neamen, D. Biswas, "Semiconductor Physics and Devices," McGraw-Hill Education.
- Electronic Devices and Circuit Theory 11th Edition by Boylestad, Robert . L, Louis Nashelskyl.
- <http://ecee.colorado.edu/~bart/book/book/contents.htm>
- <http://www.ecse.rpi.edu/~schubert/Course-ECSE-2210-Microelectronics-Technology-2010/>