
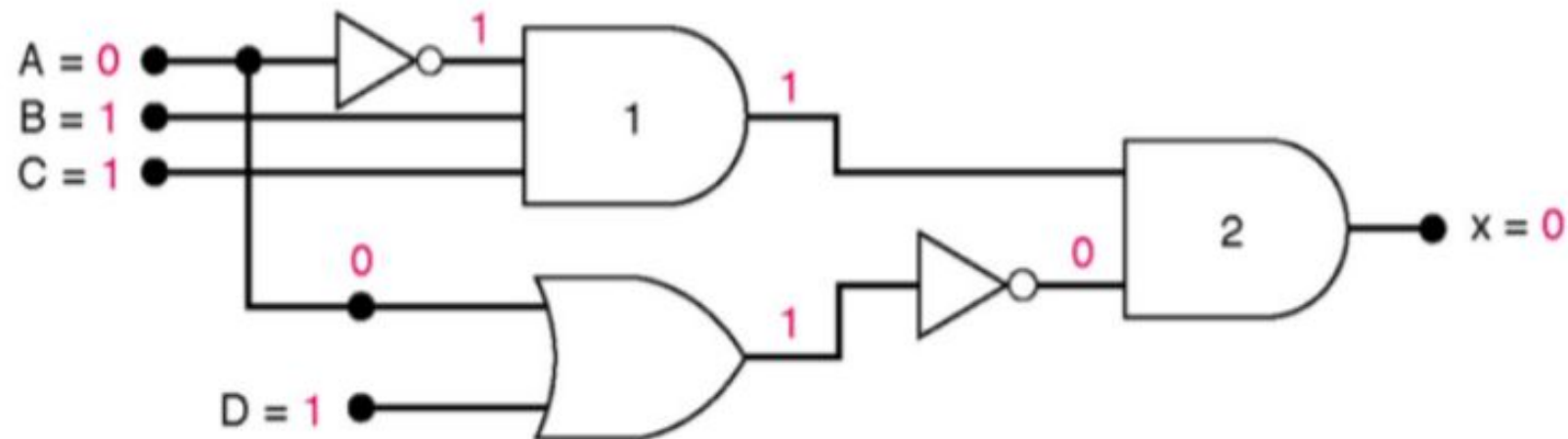



1. Boolean algebra
2. De Morgan's law
3. Positive and negative logic
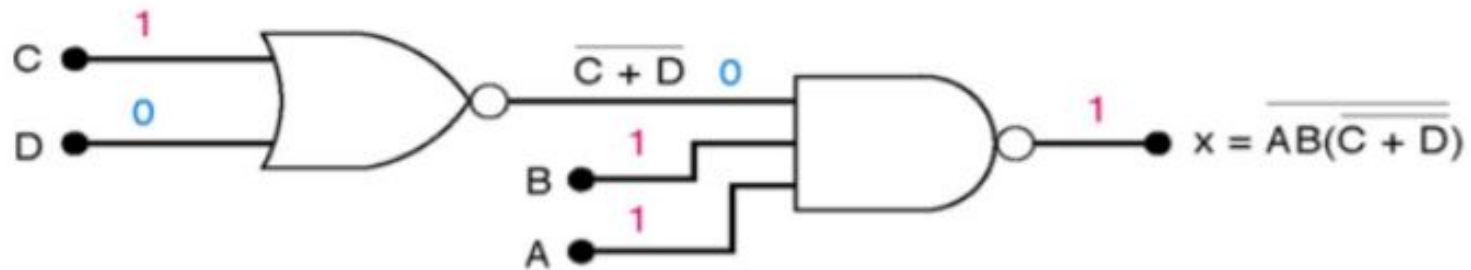
## Determining output value from a diagram


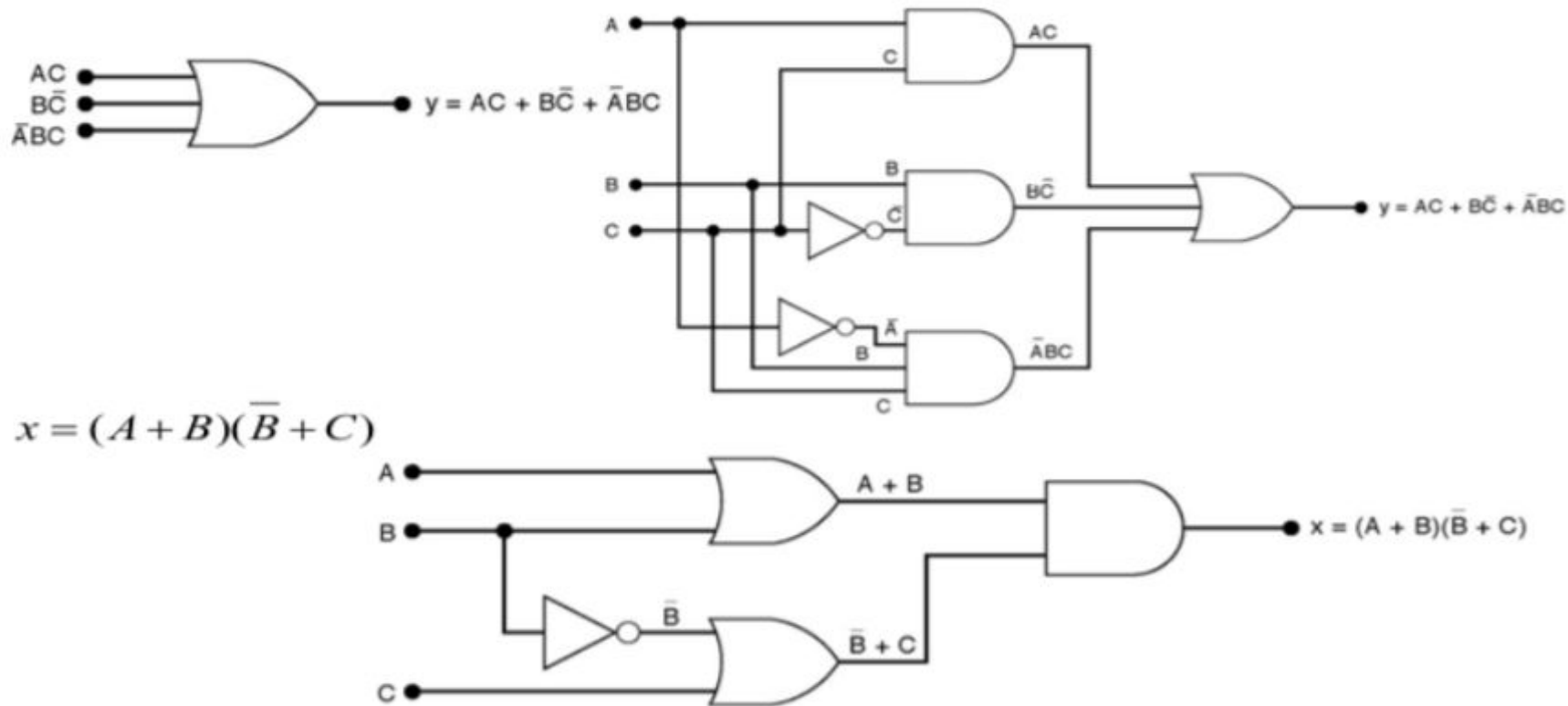
## Implementing Circuits From Boolean Expressions


- When the operation of a circuit is defined by a Boolean expression, we can draw a logic-circuit diagram directly from that expression.




# Laws of Boolean Algebra

## ◆ Commutative Laws

$$A + B = B + A$$

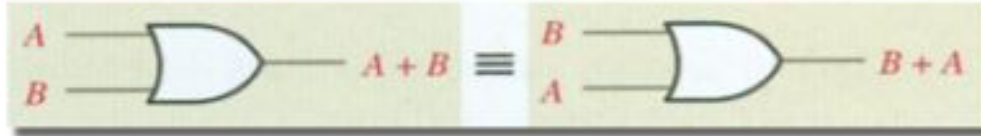


$$A \cdot B = B \cdot A$$

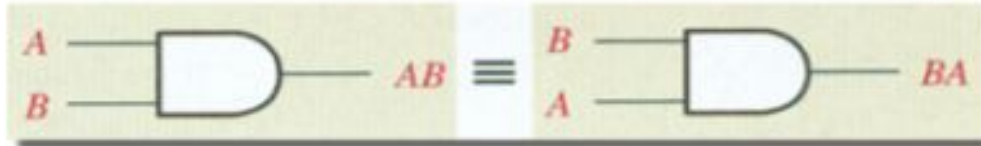


## ◆ Associative Laws

$$A + (B + C) = (A + B) + C$$

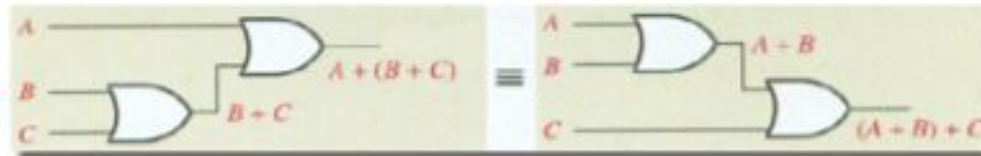

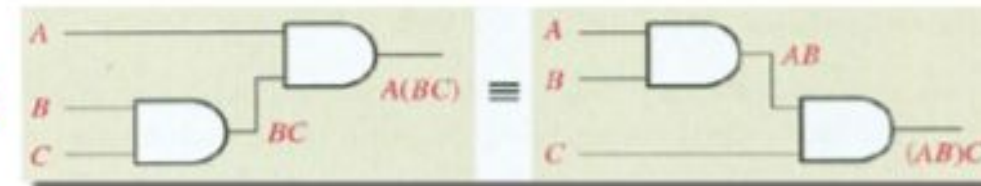
$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$



## ◆ Distributive Law

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$A(B + C) = AB + AC$$

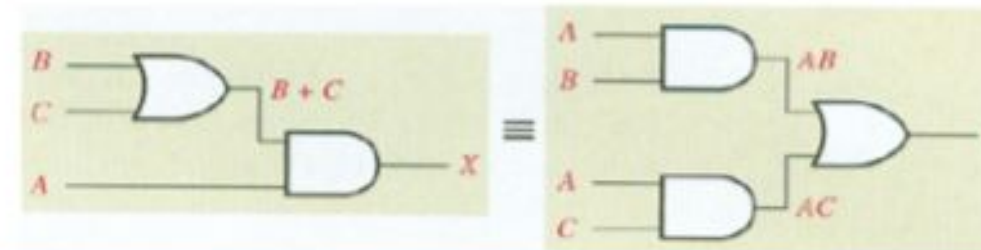

# Rules of Boolean Algebra

1.  $A + 0 = A$

2.  $A + 1 = 1$

3.  $A \cdot 0 = 0$

4.  $A \cdot 1 = A$

5.  $A + A = A$

6.  $A + \bar{A} = 1$

7.  $A \cdot A = A$

8.  $A \cdot \bar{A} = 0$

9.  $\bar{\bar{A}} = A$


10.  $A + AB = A$

11.  $A + \bar{A}B = A + B$

12.  $(A + B)(A + C) = A + BC$

- ◆ Rules 1 to 9 are obvious.
- ◆ Rule 10:  $A + AB = A$

A	B	AB	A + AB
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

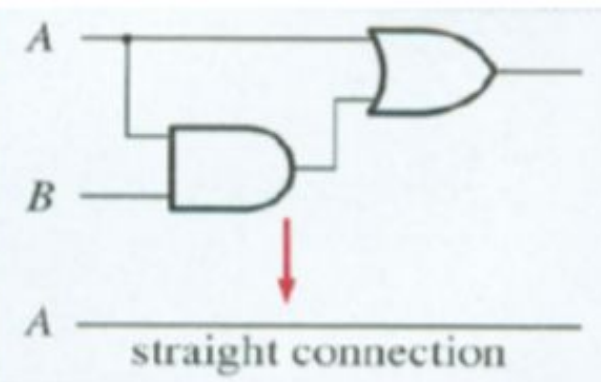




## Rules 11 and 12 of Boolean Algebra


◆ Rule 11:  $A + \overline{A}B = A + B$

A	B	$\overline{A}B$	$A + \overline{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

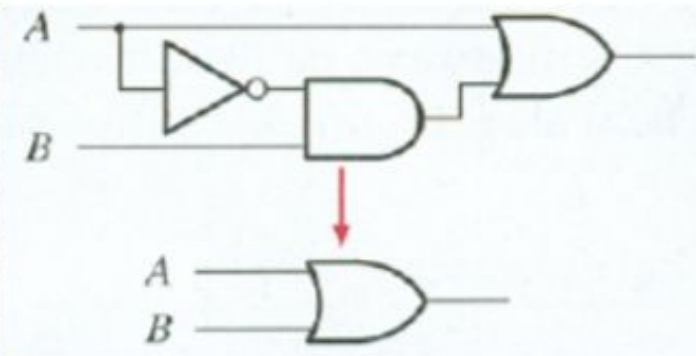

◆ Rule 12:  $(A + B)(A + C) = A + BC$

A	B	C	$A + B$	$A + C$	$(A + B)(A + C)$	$BC$	$A + BC$
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

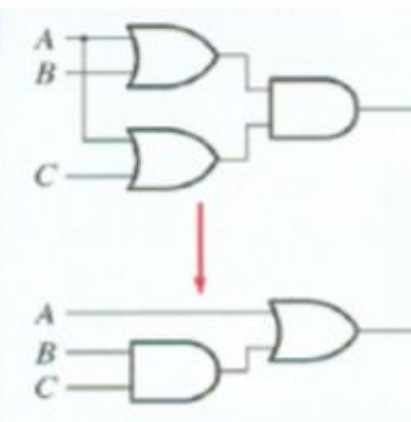

## Using Boolean Algebra to simplify expressions

---

$$y = \overline{A}BD + \overline{A}\overline{B}\overline{D} \longrightarrow y = \overline{A}\overline{B}$$

$$z = (\overline{A} + B)(A + B) \longrightarrow z = B$$

$$x = ACD + \overline{A}BCD \longrightarrow x = ACD + BCD$$

## DeMorgan's Theorems

- ◆ Theorem 1

$$\overline{(x + y)} = \bar{x} \cdot \bar{y}$$

**Remember:**

- ◆ Theorem 2

$$\overline{(x \cdot y)} = \bar{x} + \bar{y}$$

**“Break the bar,  
change the operator”**



- ◆ DeMorgan's theorem is very useful in digital circuit design
- ◆ It allows **ANDs to be exchanged with ORs by using invertors**
- ◆ DeMorgan's Theorem can be extended to any number of variables.

$$\begin{aligned} F &= \overline{X \cdot Y} + \overline{P \cdot Q} && \longleftarrow \text{2 NAND plus 1 OR} \\ &= \bar{X} + \bar{Y} + \bar{P} + \bar{Q} && \longleftarrow \text{1 OR with some input invertors} \end{aligned}$$


$$z = \overline{(\bar{A} + C) \cdot (B + \bar{D})} \longrightarrow z = A\bar{C} + \bar{B}D$$


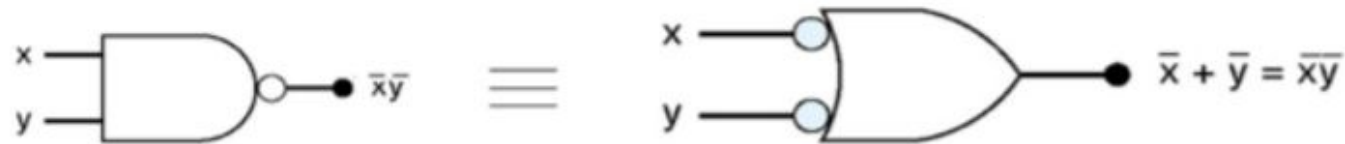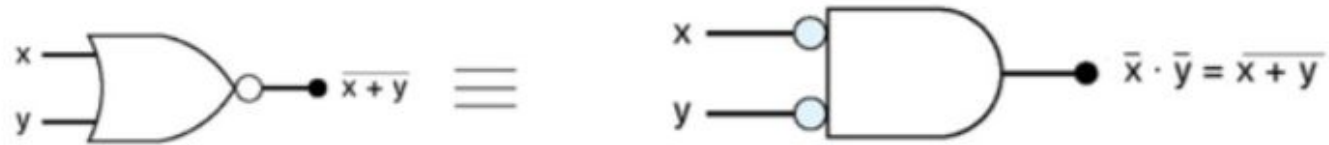
## Implications of DeMorgan's Theorems(I)



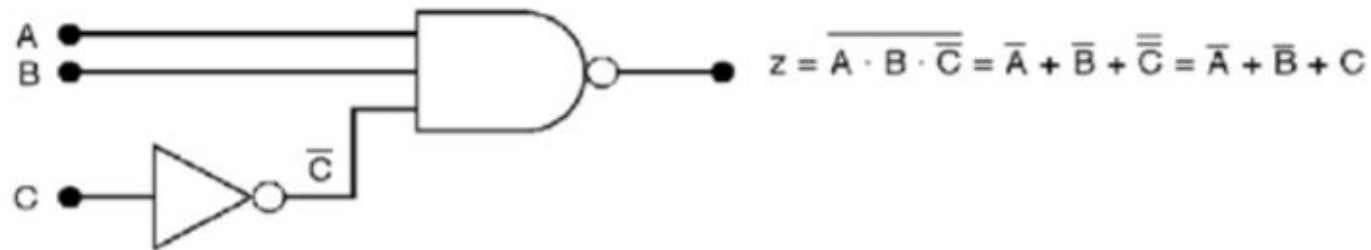- ◆ Determine the output expression for the circuit below and simplify it using DeMorgan's Theorem



## Verify De Morgan's law using Truth Table:

A	B	$\bar{A}$	$\bar{B}$	$A+B$	$A \cdot B$	$\overline{A+B}$	$\bar{A} \cdot \bar{B}$	$\overline{A \cdot B}$	$\bar{A} + \bar{B}$
0	0	1	1	0	0	1	1	1	1
0	1	1	0	1	0	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	1	0	0	0	0

# Positive and negative logic