

# Small-signal Diode Model

**Semiconductor Devices and Circuits**

**(ECE 181302)**


8<sup>th</sup> October 2021

# Diode Circuit Equations are Nonlinear

KCL : current  $i_D$  in all elements


KVL :  $v_i = Ri_D + v_D$
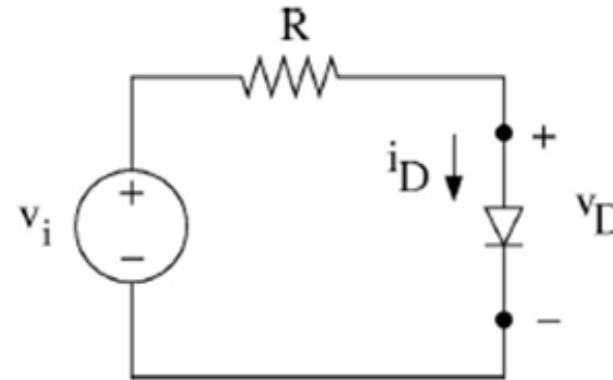
$$i_D = I_S \left( e^{v_D/nV_T} - 1 \right)$$



- Two equation in two-unknowns to solve for  $i_D$  and  $v_D$
- Non-linear equation: cannot be solved analytically
- Solution methods:
  - Numerical (PSpice)
  - Graphical (load-line)
  - Approximation to get linear equations (diode piece-linear model)

# Diode Circuit Analysis

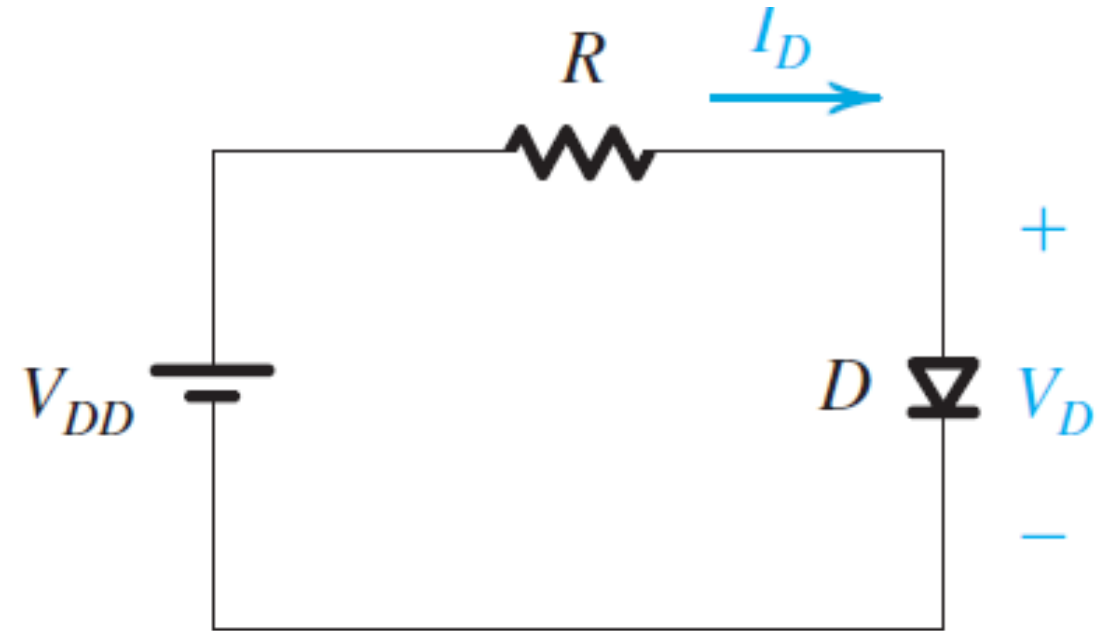


- $I_D$  and  $V_D$  can be solved using:
  - ✓ Exponential model
  - ✓ Ideal diode model
  - ✓ Constant voltage-drop model
  - ✓ Piecewise linear model

# Modeling the Diode Forward Characteristic

- Analysis of circuits employing forward conducting diodes.
- Simplified diode models are better suited for use in circuit analysis and design of diode circuits:
  - ✓ Exponential model
  - ✓ Ideal diode model
  - ✓ Constant voltage-drop model
  - ✓ Piecewise linear model
  - ✓ Small-signal (linearization) model

# Small-signal Diode Model

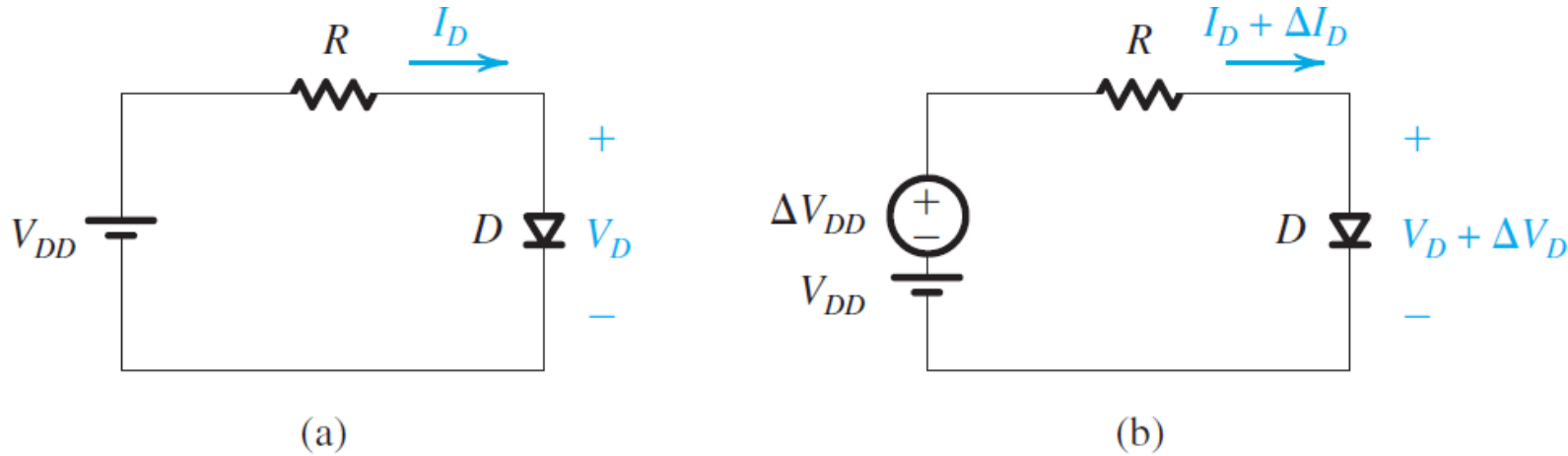


(a) A simple diode circuit; (b) the situation when  $V_{DD}$  changes by  $\Delta V_{DD}$ .

- Voltage  $V_{DD}$  undergoes a small change  $\Delta V_{DD}$ .
  - $\Delta V_{DD}$ . Is time-varying.
- Current  $I_D$  changes by an increment  $\Delta I_D$ .
- Diode voltage  $V_D$  changes by an increment  $\Delta V_D$ .


- Voltage across the diode is the sum of the dc voltage  $V_D$  and the time-varying signal  $v_d(t)$
- Total instantaneous voltage across the diode is:  $v_D(t) = V_D + v_d(t)$
- Get the total instantaneous diode current will be by substituting  $v_D$  in the diode current equation  $i_D(t) = I_S e^{v_D/V_T}$
- Therefore:

$$\begin{aligned} i_D(t) &= I_S e^{(V_D + v_d)/V_T} \\ &= I_S e^{V_D/V_T} e^{v_d/V_T} \end{aligned}$$

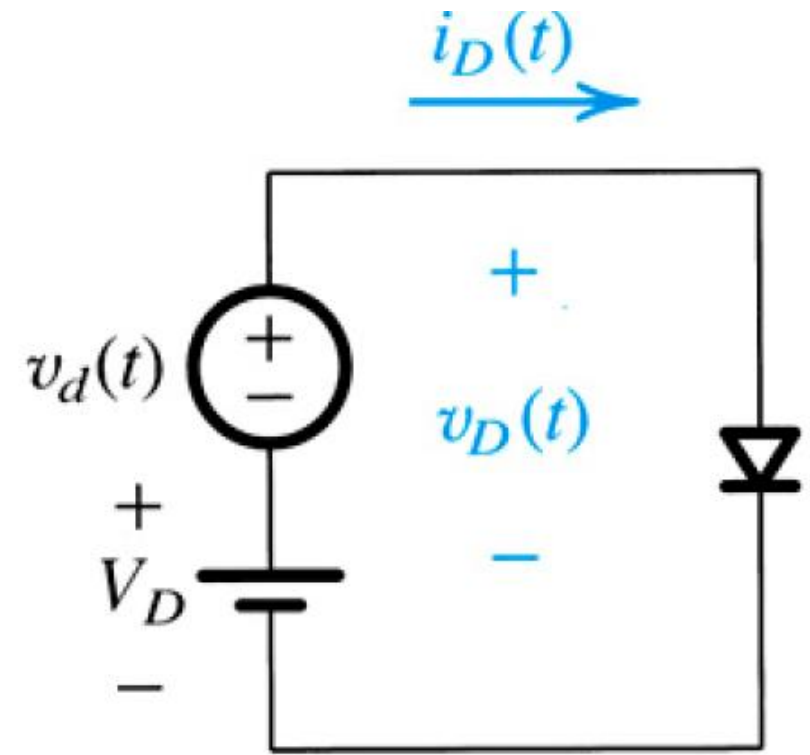- DC only – upper-case w/ upper-case subscript
- Time-varying only – lower-case w/ lower-case subscript
- Total instantaneous – lower-case w/ upper-case subscript DC + time-varying



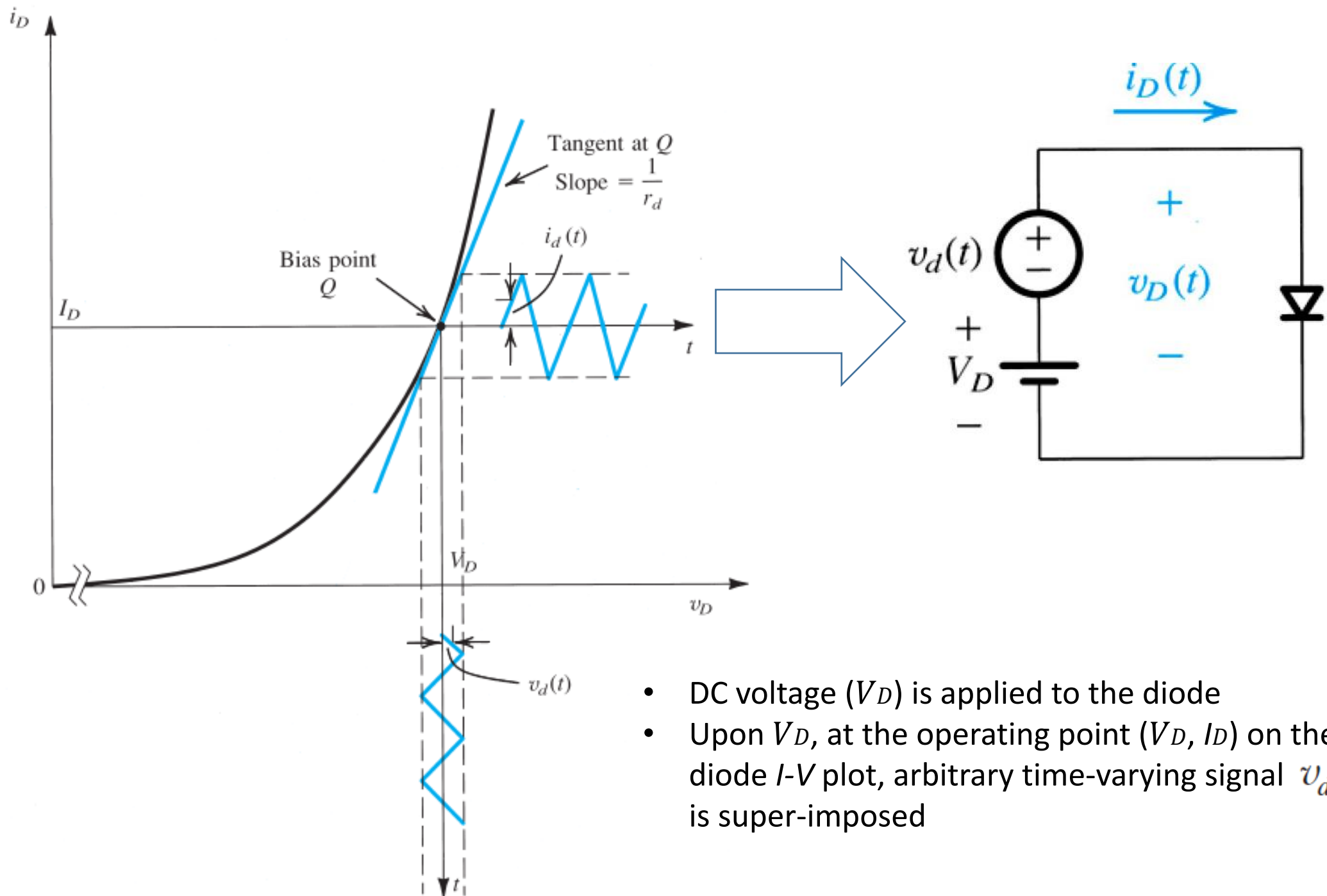Conceptual circuit of small-signal diode model



- In the absence of the signal  $v_d(t)$  the diode voltage is equal to  $V_D$ , and the diode current is  $I_D$ :

$$I_D = I_S e^{V_D/V_T}$$

- Therefore total instantaneous diode current is:  $i_D(t) = I_D e^{v_d/V_T}$

- Apply the power series expansion to the diode current:

$$i_D(t) = I_D \underbrace{\left( 1 + \frac{v_d}{V_T} + \underbrace{\left[ \left( \frac{v_d}{V_T} \right)^2 \frac{1}{2!} \right] + \left[ \left( \frac{v_d}{V_T} \right)^3 \frac{1}{3!} \right] + \dots}_{\text{power series expansion of } e^{v_d/V_T}} \right)}_{\text{apply power series expansion}}$$

because  $v_d / V_T \ll 1$ , these terms are assumed to be negligible

- Because  $\frac{v_d}{V_T} \ll 1$  higher terms are neglected and the series is truncated after the first two terms to obtain the approximate expression:

$$i_D(t) \simeq I_D \left( 1 + \frac{v_d}{V_T} \right)$$

- This is the **small-signal approximation** and it is valid for signals whose amplitudes are smaller than about 5 mV (recall that  $V_T = 25$  mV)



- Total instantaneous diode current  $i_D(t) = I_D + \frac{I_D}{V_T} v_d$
- We have a signal current component directly proportional to the signal voltage  $v_d$  superimposed on the dc current  $I_D$ , i.e.

$$i_D = I_D + i_d \quad \text{where} \quad i_d = \frac{I_D}{V_T} v_d$$

- The quantity relating the signal current  $i_d$  to the signal voltage  $v_d$  has the dimensions of conductance, mhos ( $\mathcal{U}$ ), and is called the **diode small-signal conductance**.
- The inverse of this parameter is the **diode small-signal resistance**, or **incremental resistance**,  $r_d$ ,

$$r_d = \frac{V_T}{I_D}$$

# Small-signal Resistance $r_d$


- Assuming that the signal amplitude is sufficiently small such that the excursion along the  $I$ - $V$  curve is limited to a short almost-linear segment, then

$$r_d = 1 / \left[ \frac{\partial i_D}{\partial v_D} \right]_{i_D=I_D}$$


- This method may be used to approximate any function  $y = \mathbf{f}(x)$  around an operating point  $(x_0, y_0)$ .

$$y(t) = y_0 + \left( \frac{\partial y}{\partial x} \bigg|_{y=y_0} \right)^{-1} \overbrace{(x(t) - x_0)}^{\Delta x}$$

# Small-signal Equivalent Circuit

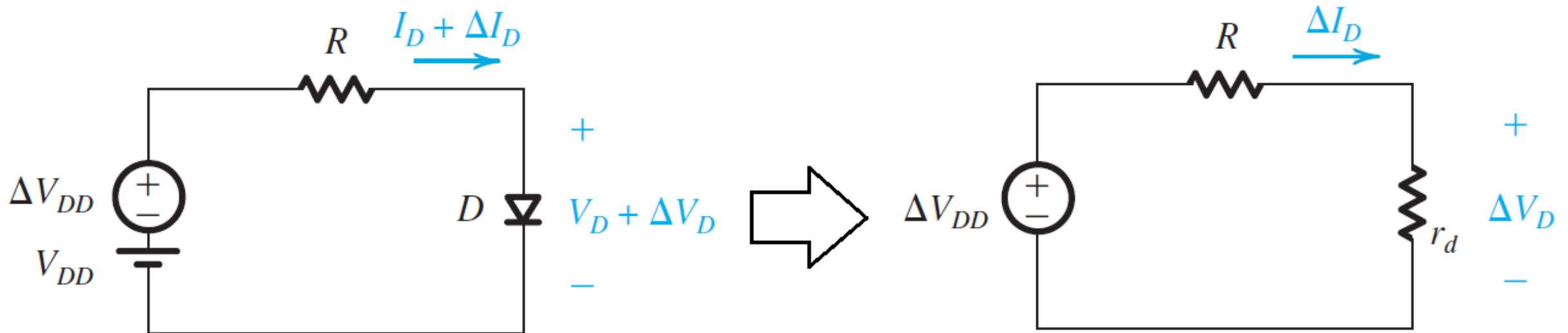

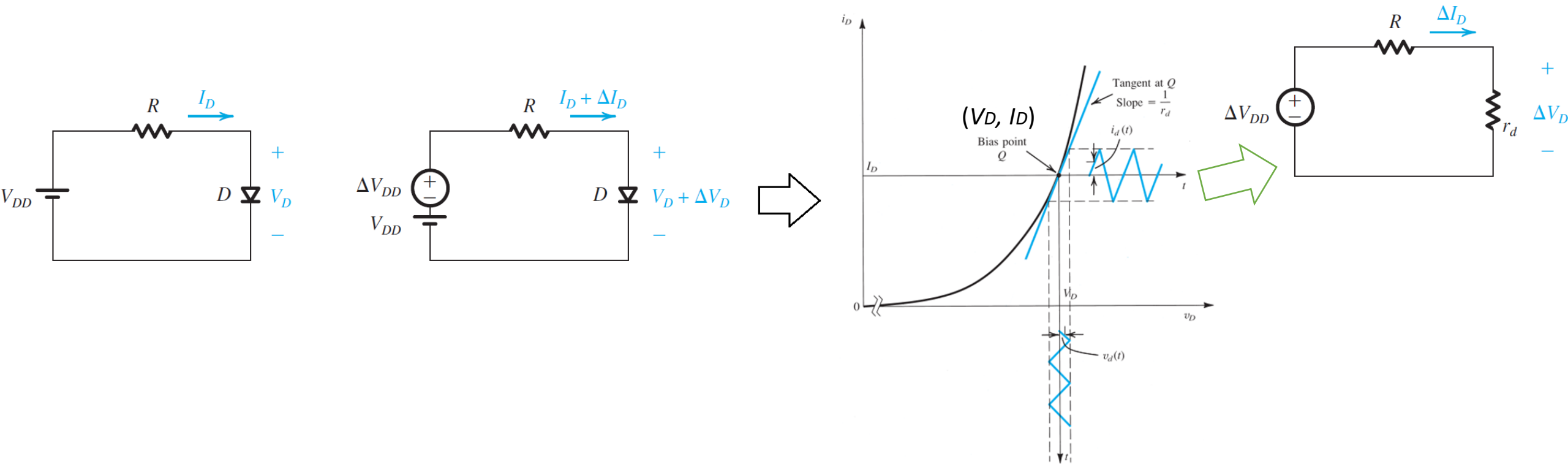- The small-signal equivalent circuit determines the incremental quantities  $I_D$  and  $V_D$  for the circuit by replacing the diode with its small-signal resistance  $r_d$  results in a linear circuit.



- Diode circuit operates at a dc biased point on the forward  $I$ - $V$  characteristic and a small ac signal superimposed on the dc.
- The dc operating point  $(V_D, I_D)$  is determined by other model (e.g. constant voltage drop model or CVDM).
- Diode small-signal is modeled as variable resistor (= inverse of the slope of the tangent to exponential  $I$ - $V$  characteristic at the bias point  $(V_D, I_D)$ ).
- Value of variable resistor is defined via linearization of exponential model around bias point defined by CVDM.

- The total instantaneous circuit is divided into steady-state and time varying components, which may be analyzed separately and solved via algebra:
  - In steady-state, diode represented as CVDM (Constant Voltage Drop Model).
  - In time-varying, diode represented as resistor.
- Neither of these circuits employ the exponential model – simplifying the “solving” process.
- Difficulty of diode circuit analysis due to nonlinear nature is avoided.



# References:

- Microelectronic Circuits, 7th edition by Adel S. Sedra Kenneth C. Smith.
- G. Streetman, and S. K. Banerjee, "Solid State Electronic Devices," 7th edition, Pearson, 2014.
- D. Neamen, D. Biswas, "Semiconductor Physics and Devices," McGraw-Hill Education.
- Electronic Devices and Circuit Theory 11th Edition by Boylestad, Robert . L, Louis Nashelskyl.
- <http://ecee.colorado.edu/~bart/book/book/contents.htm>
- <http://www.ecse.rpi.edu/~schubert/Course-ECSE-2210-Microelectronics-Technology-2010/>