



BJT Small-Signal Analysis

Semiconductor Devices and Circuits
(ECE 181302)

24th December 2021

BJT AC Analysis Steps

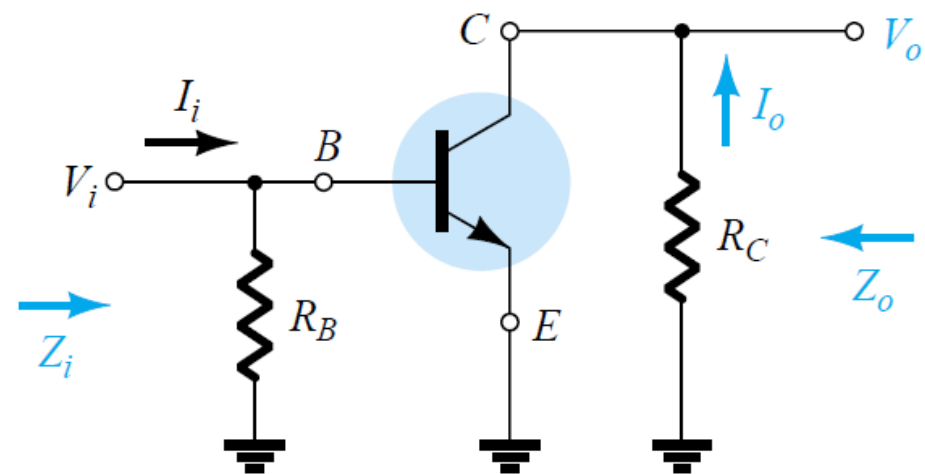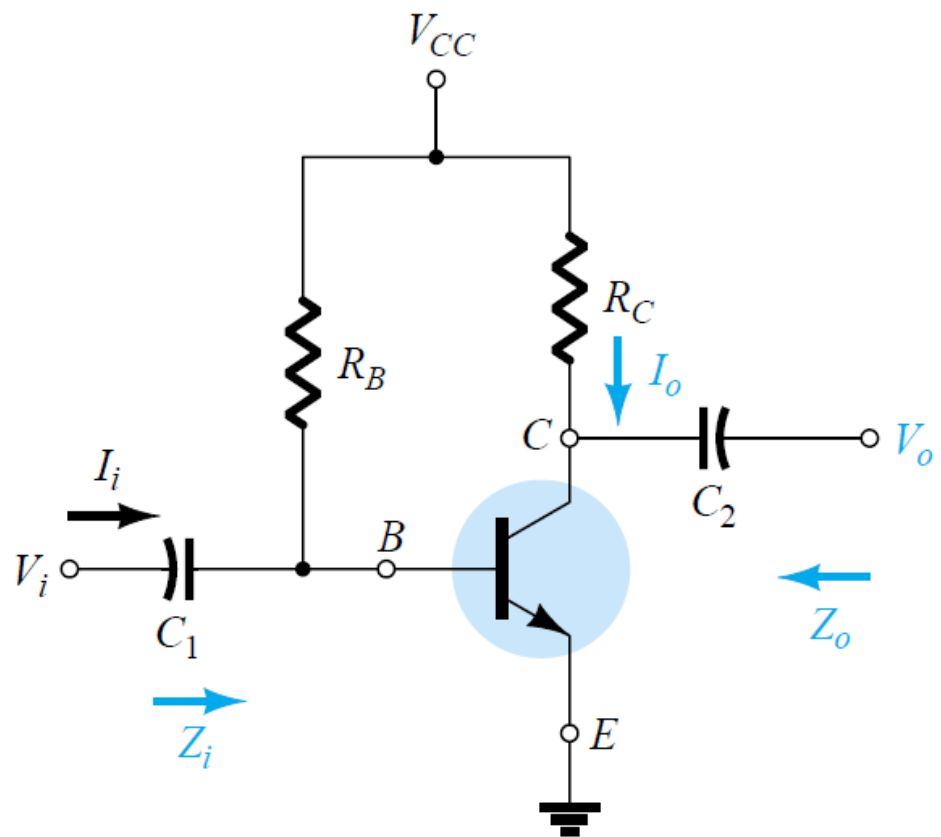- Mark the terminals of the transistor.
- Mark the current directions and define the voltages.
- Remove the dc effects of V_{CC} by connecting it to the ground.
- Ground V_{CC} .
- Replace the dc blocking capacitors by short-circuit equivalents.
- Redraw the circuit.





BJT r_e Model



- Substitute the BJT by the r_e model into the network.
- The r_e model employs a diode and controlled current source to duplicate the behavior of a transistor in the region of interest.
- The ac resistance of a diode can be determined by the equation $r_{ac} = 26 \text{ mV}/I_D$, where I_D is the dc current through the diode at the Q (quiescent) point. This same equation is used to find the ac resistance of the diode in the BJT
- Substituting the emitter current:

$$r_e = \frac{26 \text{ mV}}{I_E}$$

- The subscript e of r_e is chosen to emphasize that it is the dc level of emitter current that determines the ac level of the resistance of the diode.

CE *re* Model

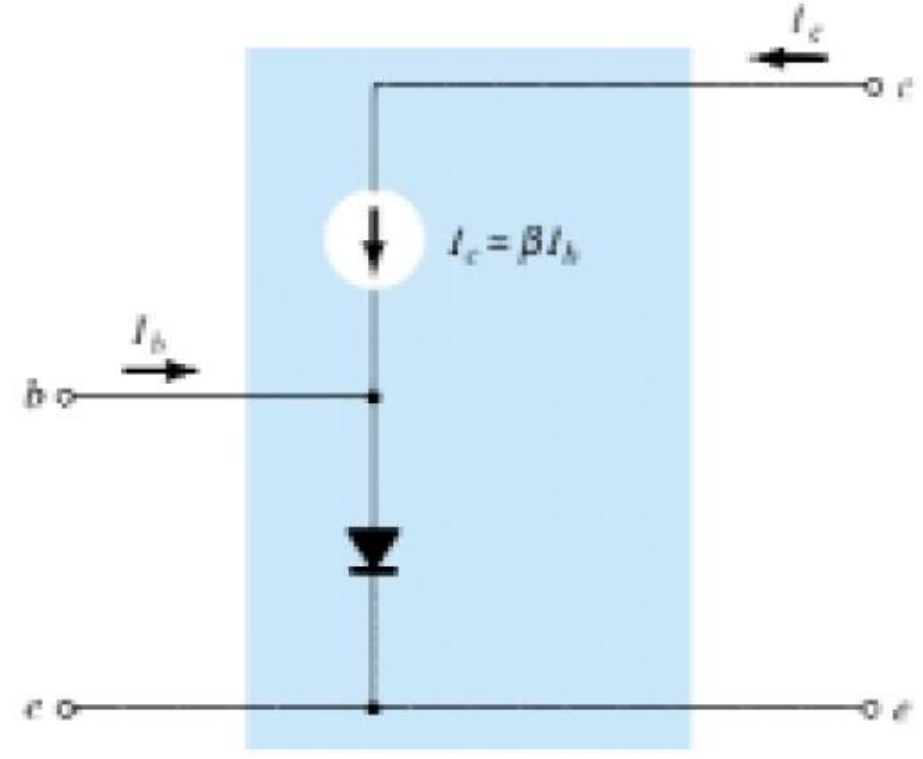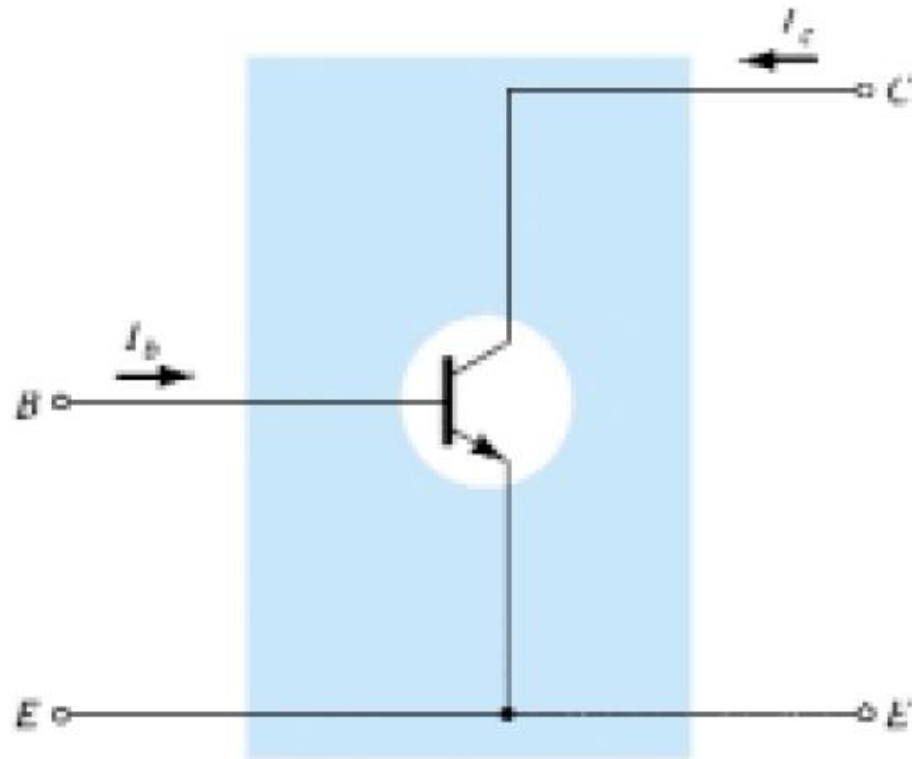

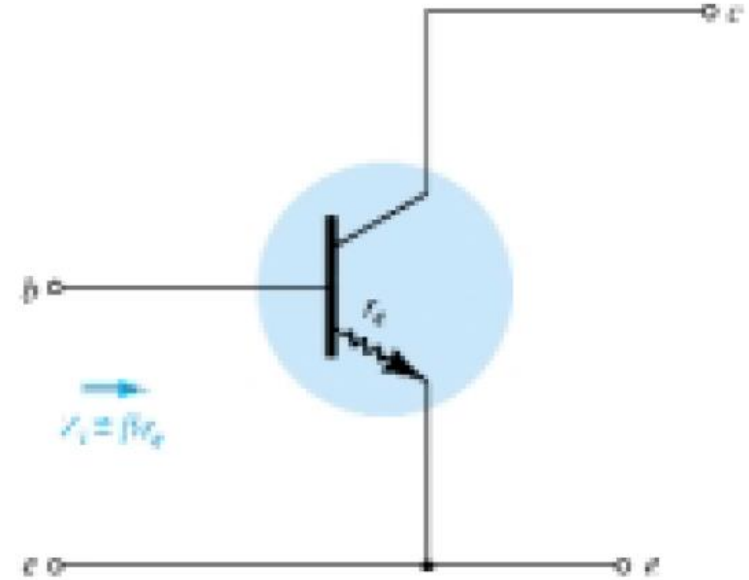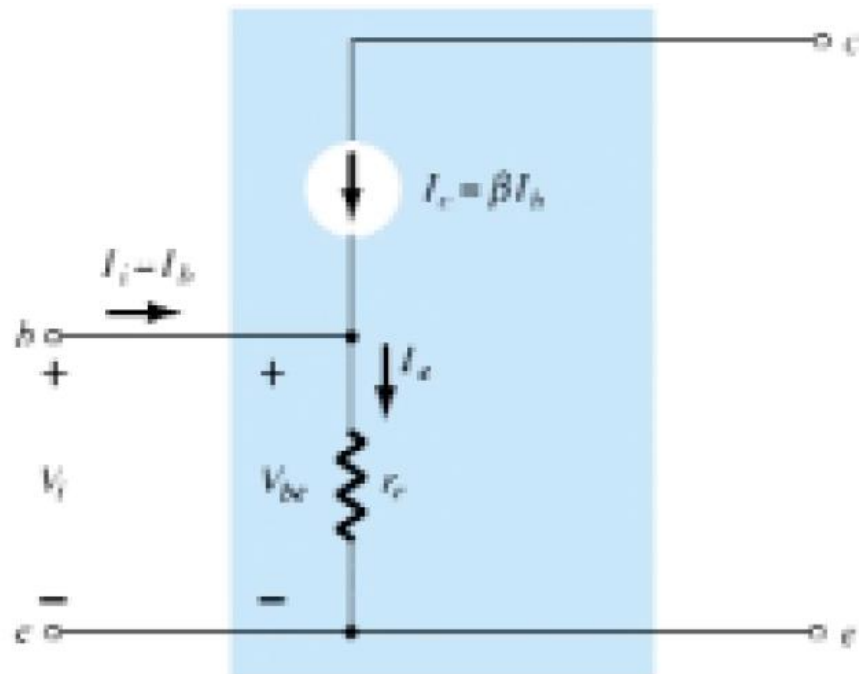

$$I_c = \beta I_b$$

$$I_e = I_c + I_b = \beta I_b + I_b$$

$$I_e = (\beta + 1)I_b$$



$$I_e \cong \beta I_b$$

$$Z_i = \frac{V_i}{I_i} = \frac{V_{be}}{I_b}$$

$$V_i = V_{be} = I_e r_e \cong \beta I_b r_e$$

$$= \frac{V_{be}}{I_b} \cong \frac{\beta I_b r_e}{I_b}$$
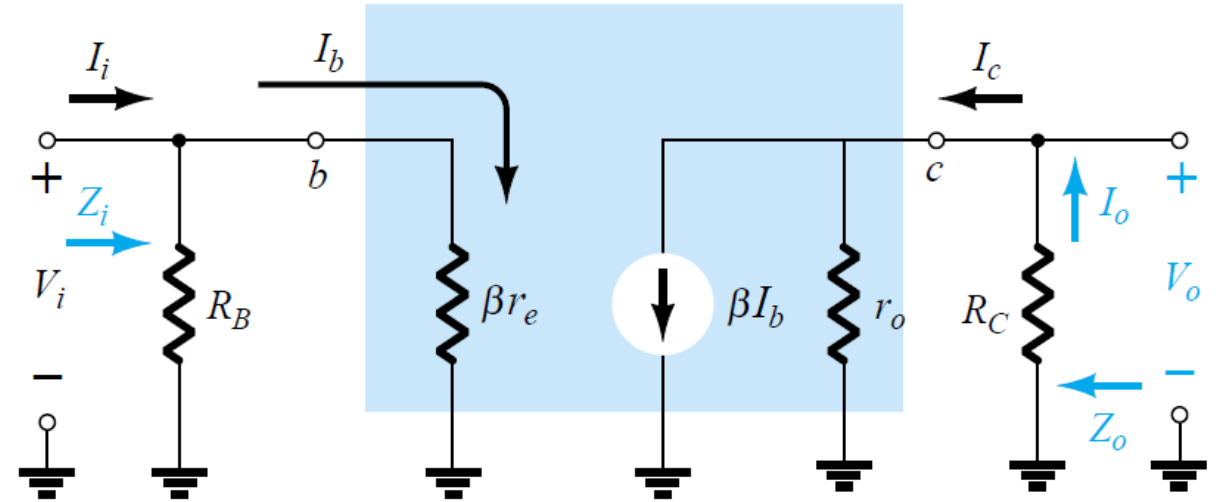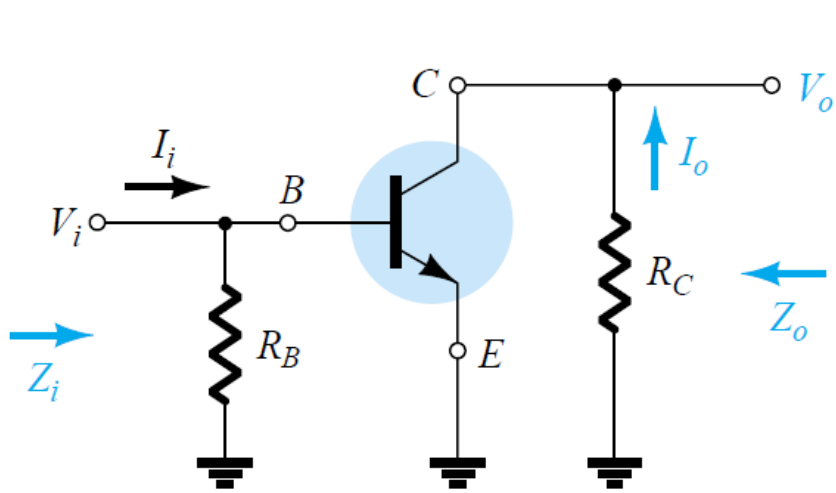
$$\boxed{Z_i \cong \beta r_e}_{CE} = (160)(6.5 \, \Omega) = \mathbf{1.04 \, k\Omega}$$



$$Z_i = R_B \parallel \beta r_e \quad \text{ohms} \quad \text{Or}$$

$$Z_i \cong \beta r_e \quad R_B \geq 10\beta r_e$$


- Z_o : The output impedance of any system is defined as the impedance Z_o determined when $V_i = 0$. When $V_i = 0$, $I_i = I_b = 0$, resulting in an open-circuit equivalence for the current source. Therefore;


$$Z_o = R_C \parallel r_o \quad \text{ohms}$$

$$Z_o \cong R_C \quad r_o \geq 10R_C$$

Example: For the network;

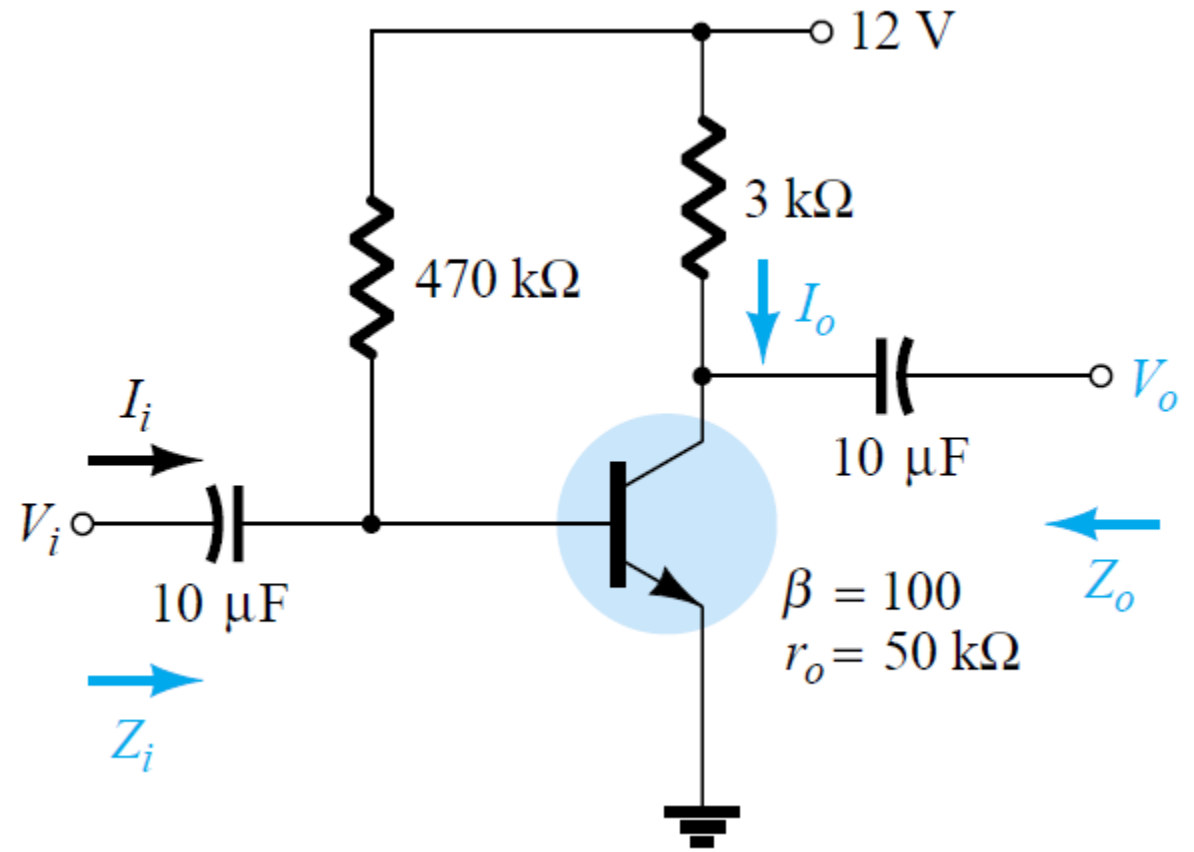- (a) Determine r_e .
- (b) Find Z_i (with $r_o = \infty\Omega$).
- (c) Calculate Z_o (with $r_o = \infty\Omega$).
- (d) Determine A_v (with $r_o = \infty\Omega$).
- (e) Find A_i (with $r_o = \infty\Omega$).
- (f) Repeat parts (c) through (e) including $r_o = 50\text{ k}\Omega$ in all calculations and compare results.



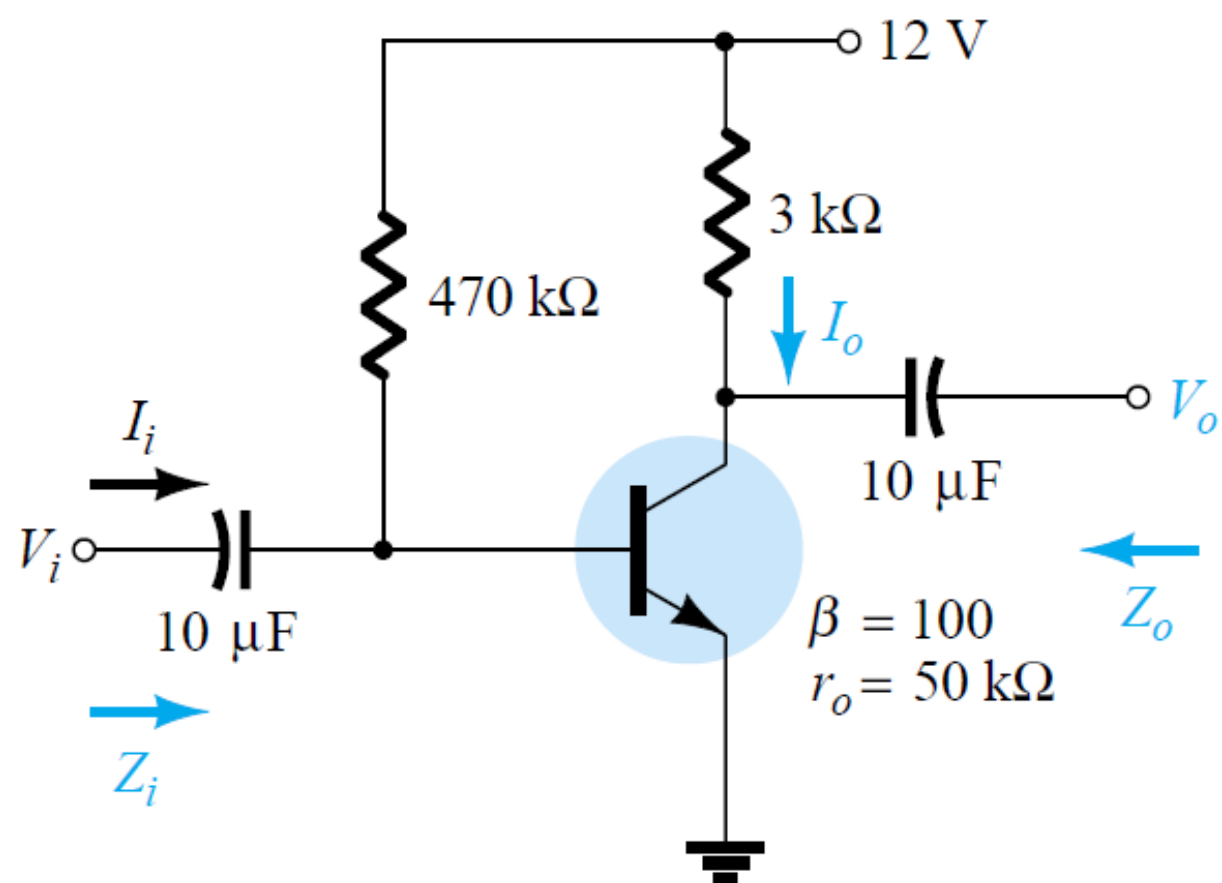

- Solution:

(a) DC analysis:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{470 \text{ k}\Omega} = 24.04 \text{ }\mu\text{A}$$

$$I_E = (\beta + 1)I_B = (101)(24.04 \text{ }\mu\text{A}) = 2.428 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{2.428 \text{ mA}} = \mathbf{10.71 \text{ }\Omega}$$

(b) $\beta r_e = (100)(10.71 \text{ }\Omega) = 1.071 \text{ k}\Omega$

$$Z_i = R_B \parallel \beta r_e = 470 \text{ k}\Omega \parallel 1.071 \text{ k}\Omega = \mathbf{1.069 \text{ k}\Omega}$$

(c) $Z_o = R_C = \mathbf{3 \text{ k}\Omega}$

(d) $A_v = -\frac{R_C}{r_e} = -\frac{3 \text{ k}\Omega}{10.71 \text{ }\Omega} = \mathbf{-280.11}$

(e) Since $R_B \geq 10\beta r_e (470 \text{ k}\Omega > 10.71 \text{ k}\Omega)$

$$A_i \cong \beta = \mathbf{100}$$

$$(f) \quad Z_o = r_o \parallel R_C = 50 \text{ k}\Omega \parallel 3 \text{ k}\Omega = \mathbf{2.83 \text{ k}\Omega} \text{ vs. } 3 \text{ k}\Omega$$

$$A_v = -\frac{r_o \parallel R_C}{r_e} = \frac{2.83 \text{ k}\Omega}{10.71 \text{ }\Omega} = \mathbf{-264.24} \text{ vs. } -280.11$$

$$A_i = \frac{\beta R_B r_o}{(r_o + R_C)(R_B + \beta r_e)} = \frac{(100)(470 \text{ k}\Omega)(50 \text{ k}\Omega)}{(50 \text{ k}\Omega + 3 \text{ k}\Omega)(470 \text{ k}\Omega + 1.071 \text{ k}\Omega)} \\ = \mathbf{94.13} \text{ vs. } 100$$

$$A_i = -A_v \frac{Z_i}{R_C} = \frac{-(-264.24)(1.069 \text{ k}\Omega)}{3 \text{ k}\Omega} = \mathbf{94.16}$$



References:

- Microelectronic Circuits, 7th edition by Adel S. Sedra Kenneth C. Smith.
- G. Streetman, and S. K. Banerjee, "Solid State Electronic Devices," 7th edition, Pearson, 2014.
- D. Neamen, D. Biswas, "Semiconductor Physics and Devices," McGraw-Hill Education.
- Electronic Devices and Circuit Theory 11th Edition by Boylestad, Robert . L, Louis Nashelskyl.
- <http://ecee.colorado.edu/~bart/book/book/contents.htm>
- <http://www.ecse.rpi.edu/~schubert/Course-ECSE-2210-Microelectronics-Technology-2010/>